




ARFTG Workshop, Boulder, December 2014



Design and measurements of high-efficiency PAs with high PAR signals

*Zoya Popovic, Tibault Reveyrand, David Sardin, Mike Litchfield, Scott
Schafer, Andrew Zai*

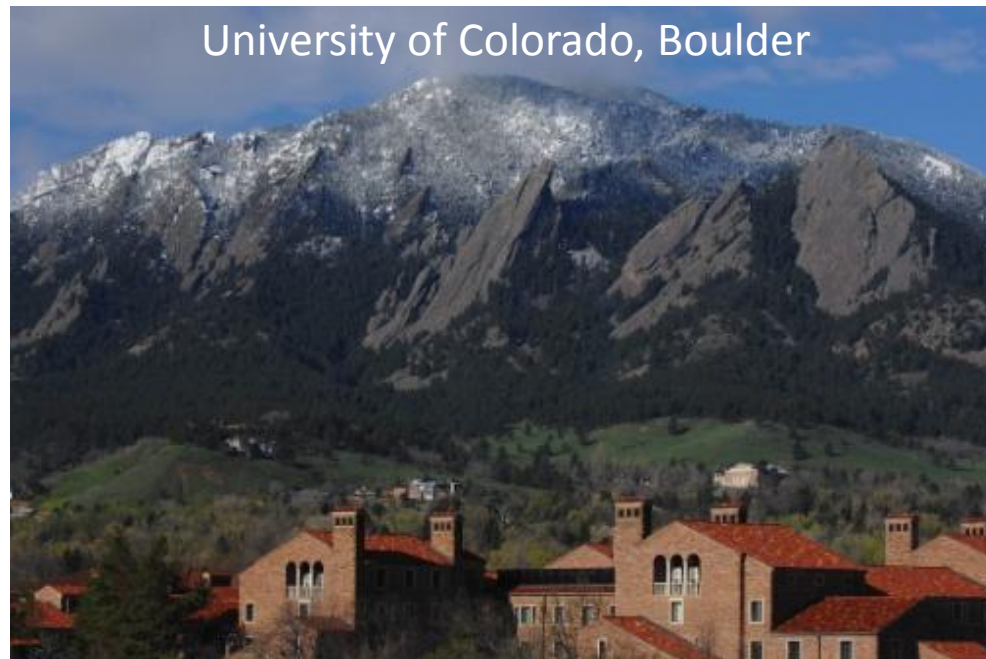Department of Electrical, Computer and Energy Engineering








Main challenges in PA design



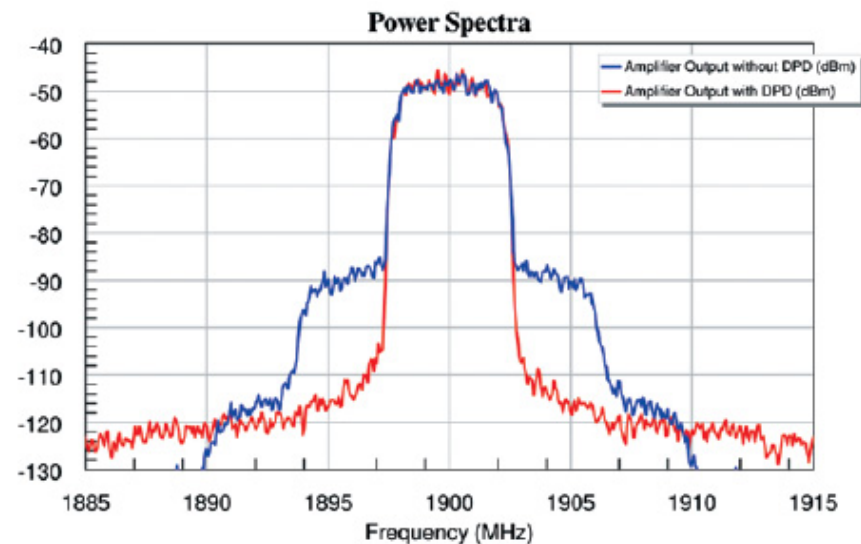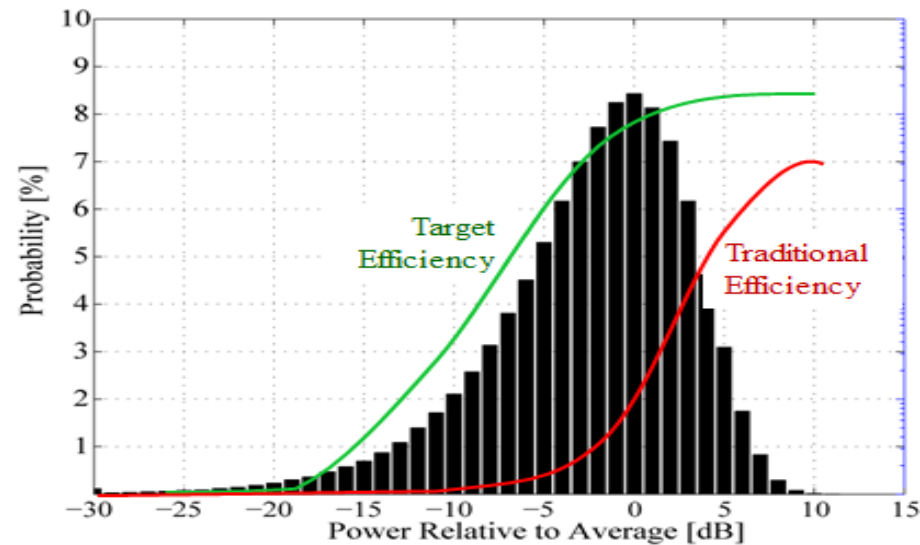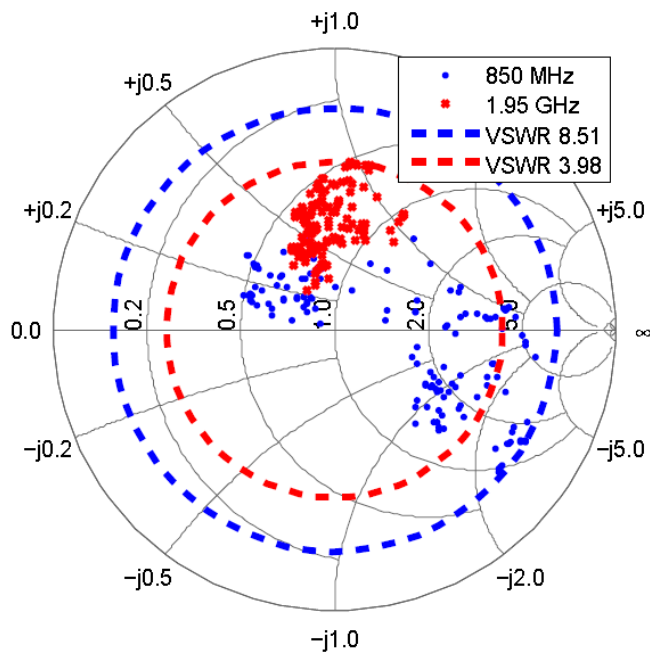- Challenge 1: efficiency drops as output power drops
- Challenge 2: efficient PAs are nonlinear
- Challenge 3: load can vary





Outline




- **Overview of approaches for improving efficiency at power back-off**
- Supply modulation
 - GaN PA design (10GHz carrier)
 - Supply modulator (100MHz switching)
 - Integration and modeling
- Outphasing
 - Quasi-MMIC isolated and non-isolated
 - Measurements of load modulation internal to the PA
 - Outphasing with supply modulation
- Discussion and some other challenges



Transmitter architectures



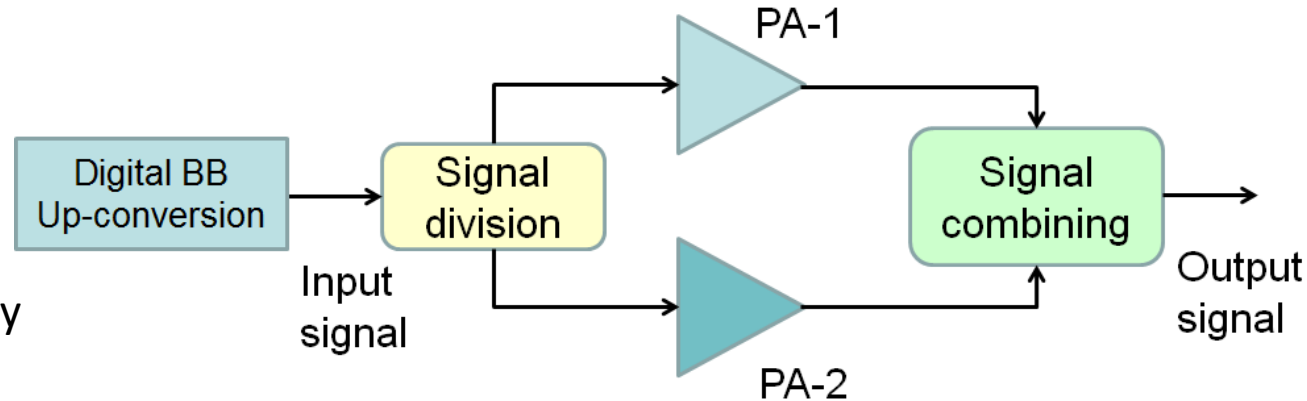- Doherty PAs
 - Main and peaking RFPAs
 - Digital drive
 - Combined with supply modulation
- Supply modulation (ET...)
 - Various methods
 - One RFPAs, lower frequency PA, dc-dc converter(s)
- Outphasing (LINC, Chireix)
 - Two saturated RFPAs
 - Digital pre-processing
 - Combined with supply modulation




- Need second amplifier of some sort, complexity increases
- Is the added complexity worth it?




Doherty PAs



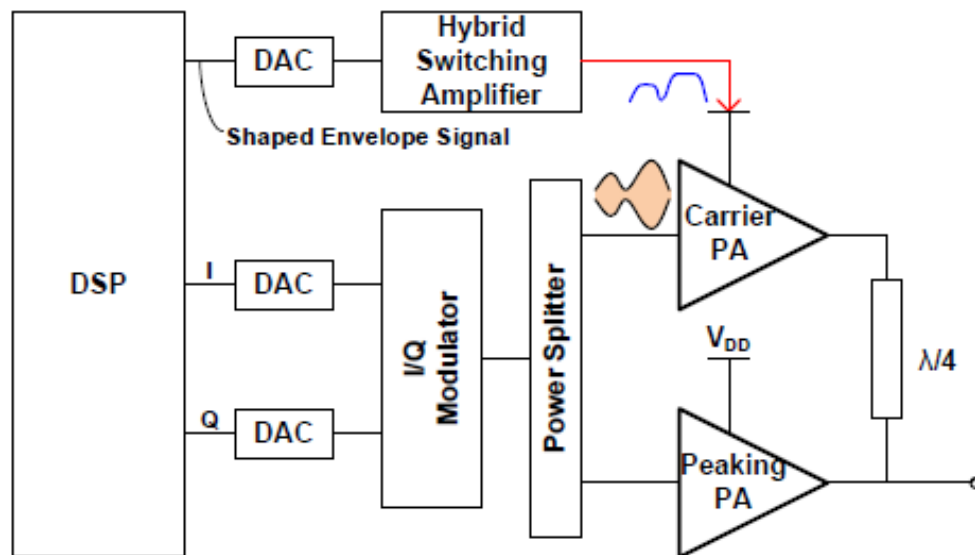- Limitations: broadband signals; efficiency in back-off limited (class AB-B)
- Non-ideal peaking amplifier current turn-on characteristics
- Needs linearization although carrier PA is in principal linear
- Currently ~60% peak, 40% average for WCDMA and LTE, 2GHz




From B. Kim et al, 2010

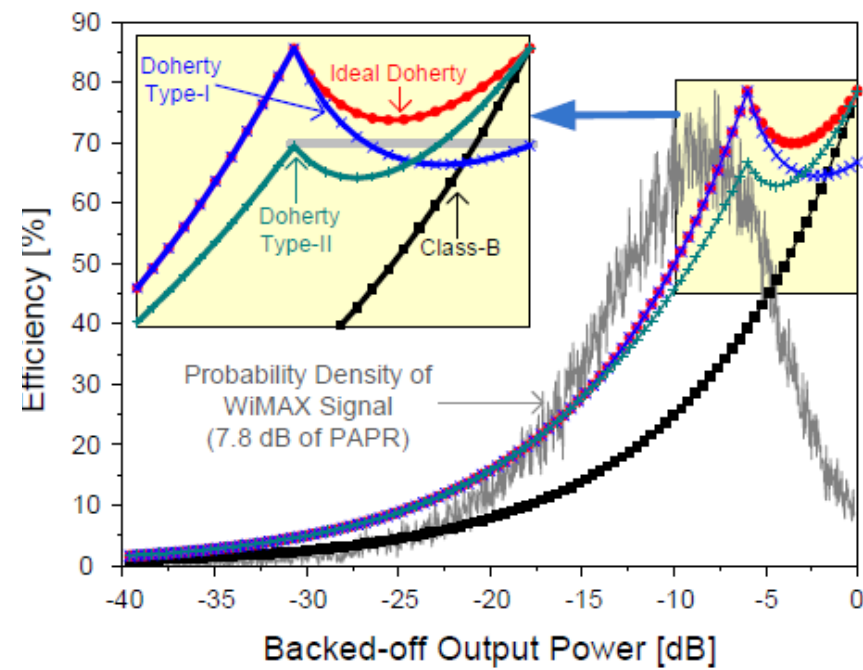



Outphasing (LINC) PAs

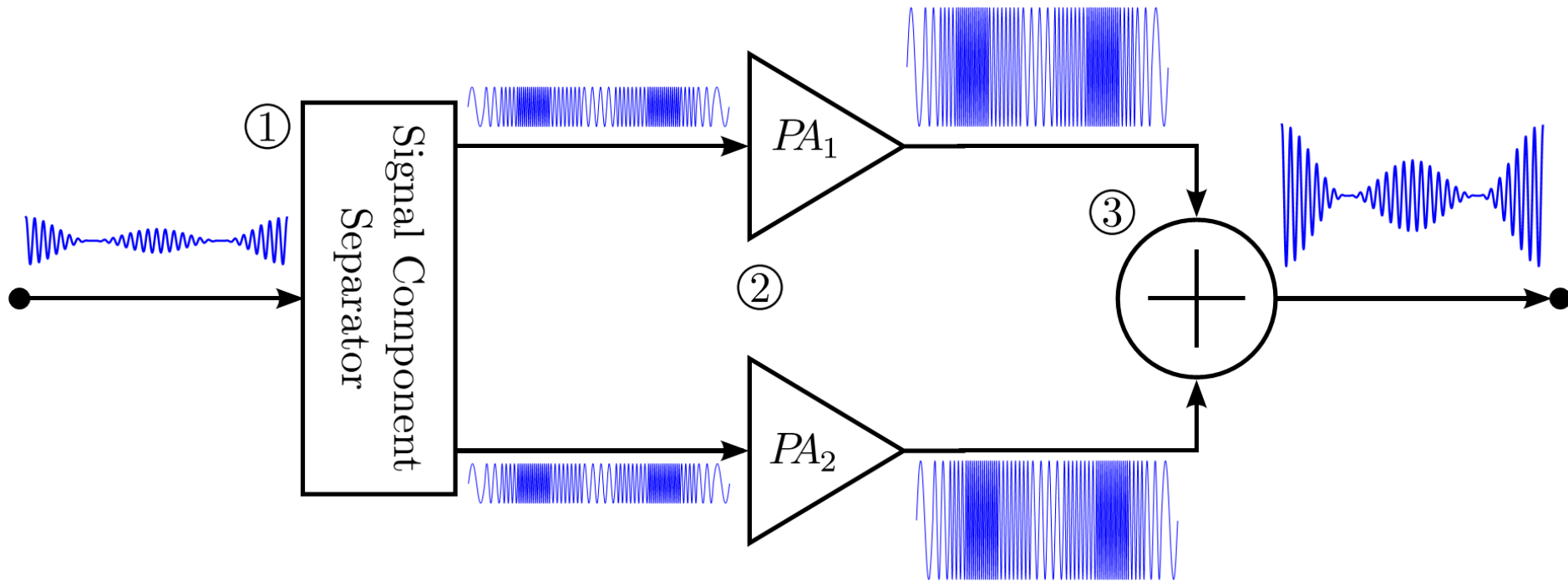



- Amplitude modulation converted to additional phase modulation
- High-efficiency PAs driven with constant envelope
- Combiner reconstructs envelope through vector addition
- Combiner can be isolated or non-isolated



Supply Modulation (ET)



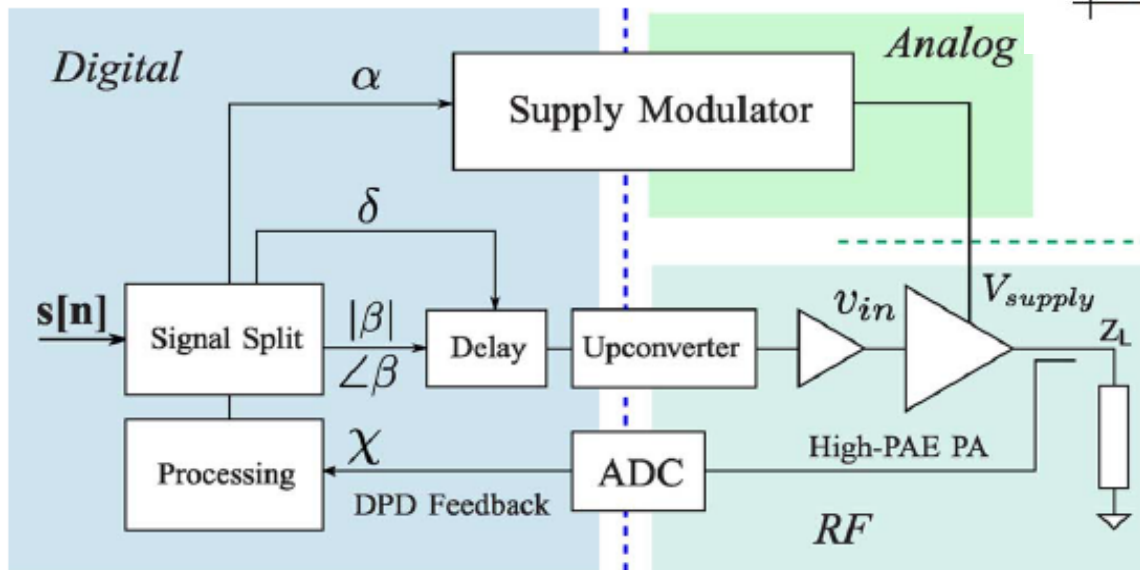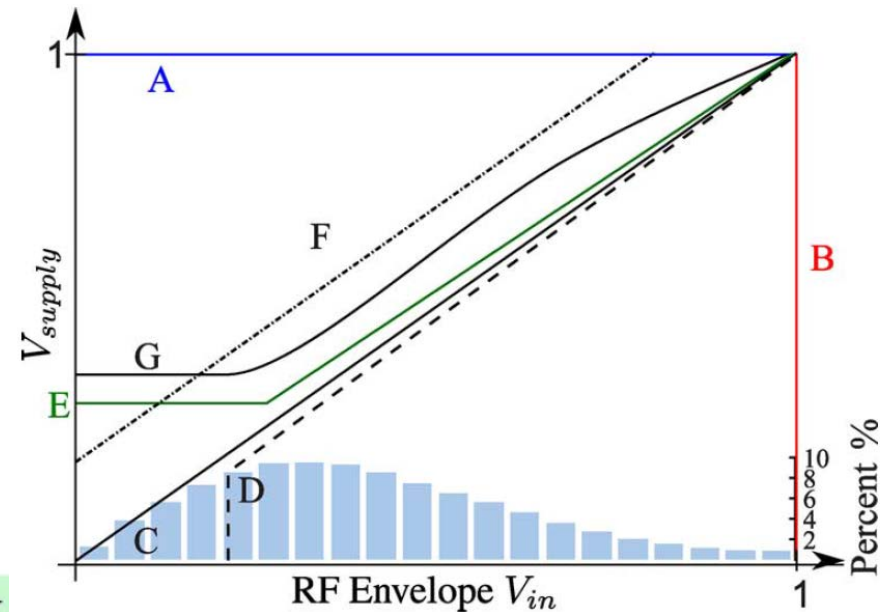- Various names used in the literature: EER, ET, polar, PDM, WBET, HQPM, HEER, DDVB...
- PAs designed as AB, E, F, F-1, C, J...



Need:

- Efficient RFPA
- Efficient supply modulator
- Linearization





PAs with Supply Modulation



Challenges:




- High-efficiency PA design over large range of drain bias
- High-efficiency envelope-bandwidth supply modulator design
- Dynamic loading between PA and supply modulator
- Various forms of distortion

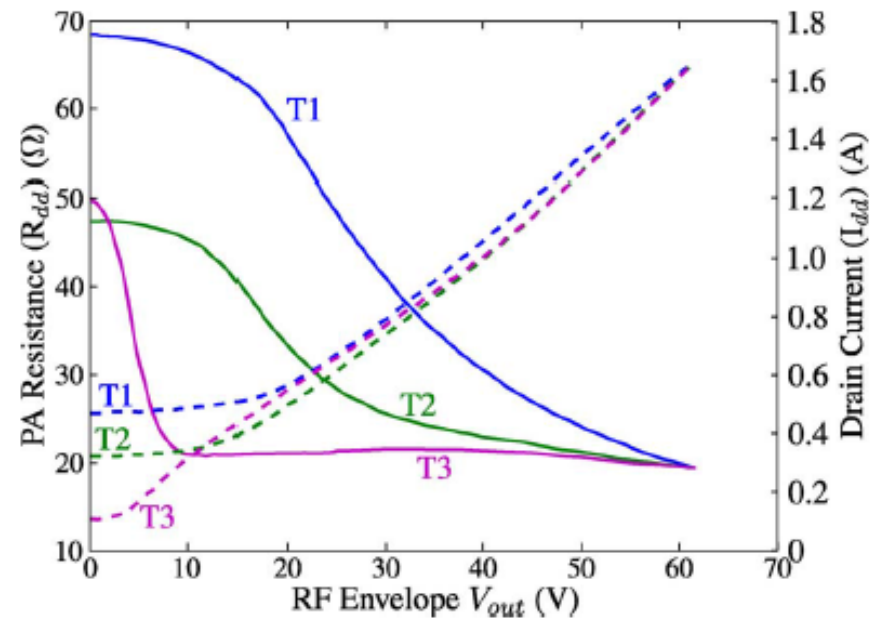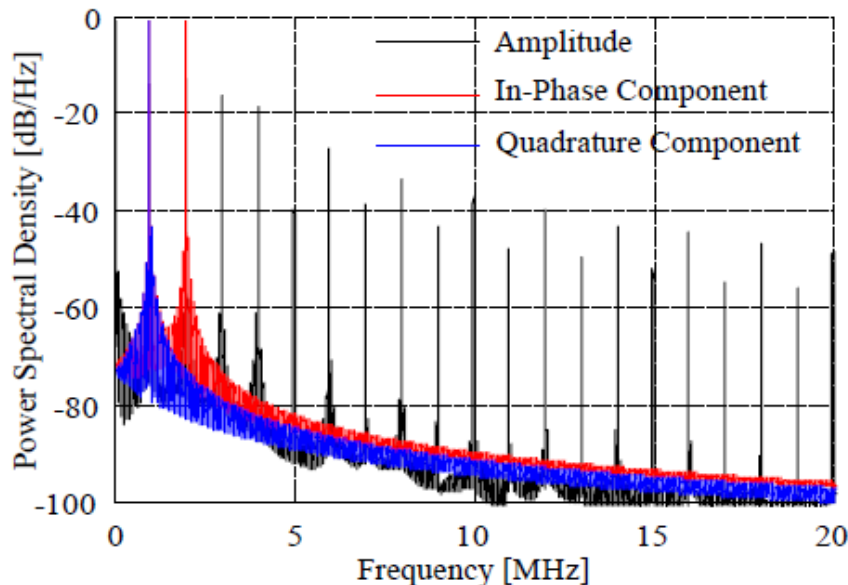Benefit: heat distributed between PA and SM






High-efficiency PA design

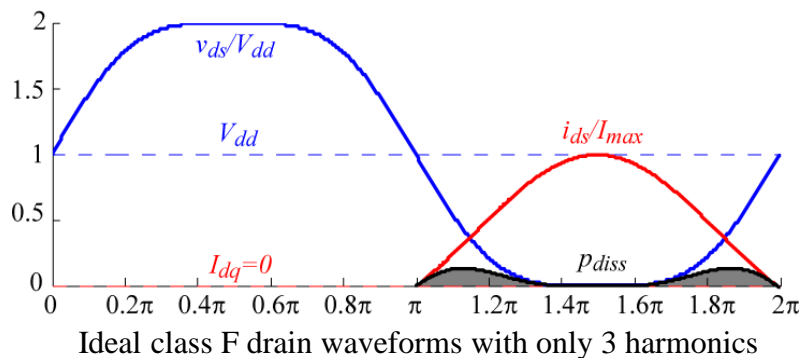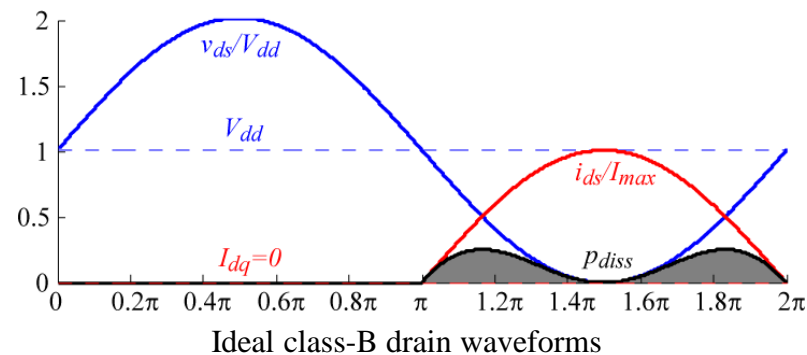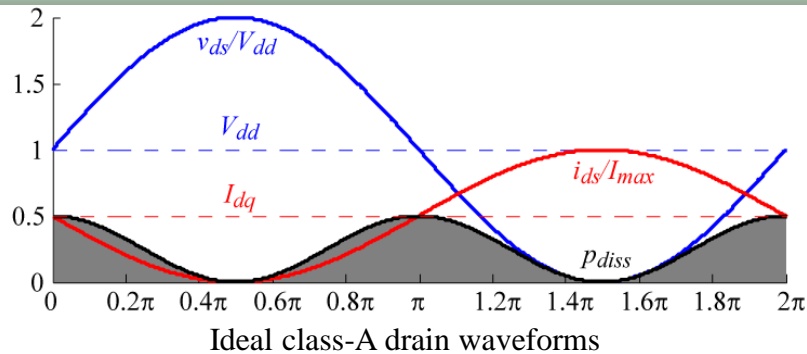





$$PAE = \frac{P_{out} - P_{in}}{P_{dd}}$$

$$\eta_d = \frac{P_{out}}{P_{dd}}$$

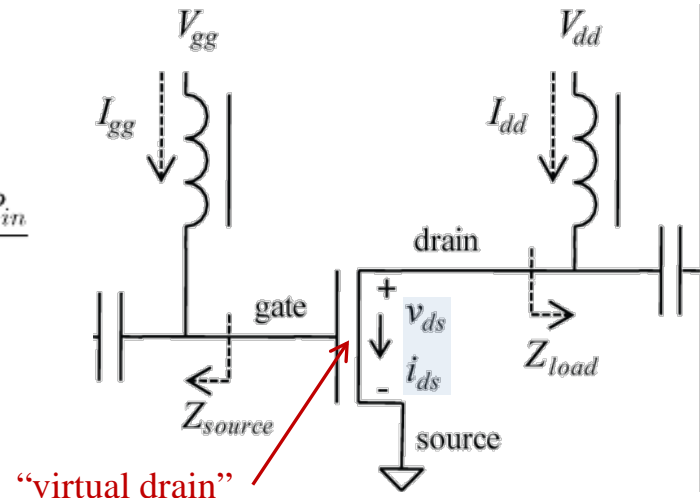

- Transistor power dissipation dominates
 - Reduced conduction angle
 - Avoids v_{ds} - i_{ds} overlap, power dissipation
- Waveform shaping (e.g. class F)
 - Voltage squaring, current peaking
 - 2nd harmonic short allows $2f_o$ current
 - 3rd harmonic open allows $3f_o$ voltage

Effects of 2nd and 3rd harmonic

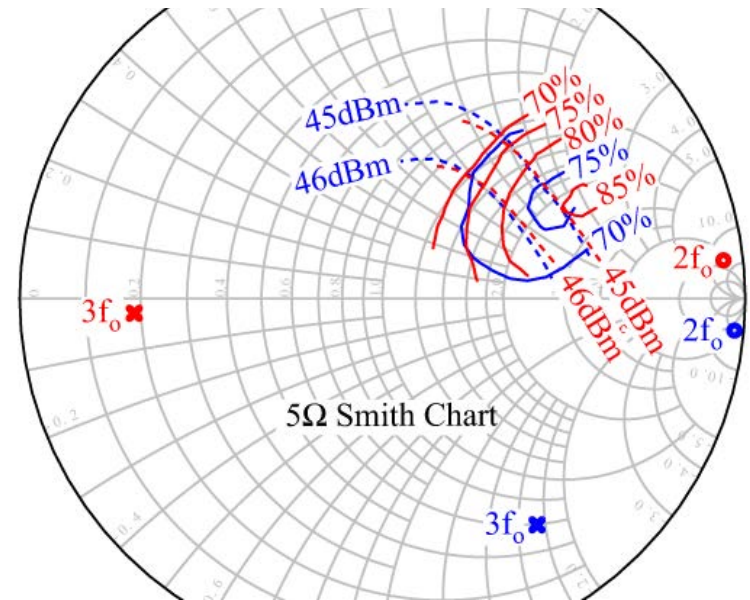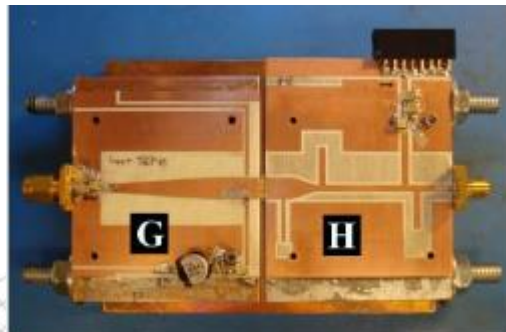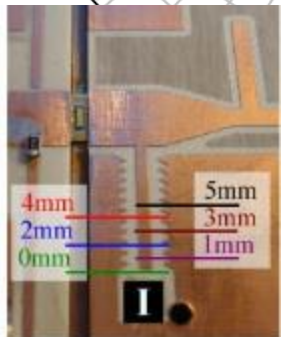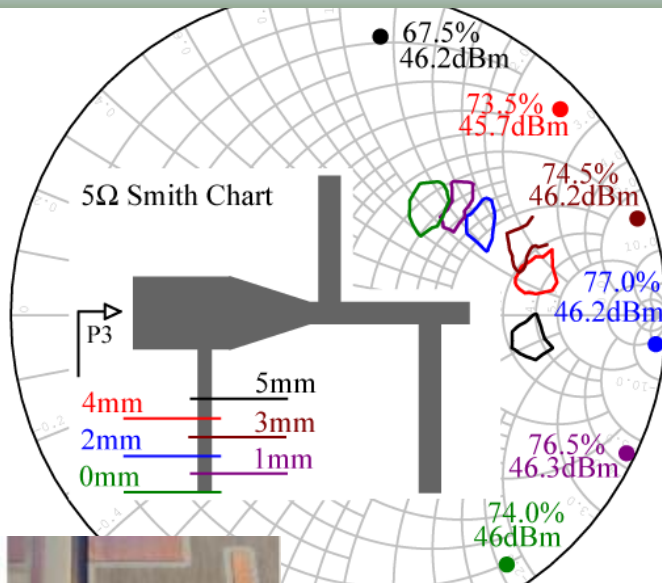

2nd harmonic and 2nd/3rd harmonic load pull for the TGF2023-10 GaN HEMT in chip/wire configuration biased at 28V drain voltage and with 300mA quiescent current.

| | 2 nd Harmonic | 2 nd /3 rd Harmonic |
|------------------|--------------------------|---|
| Output Power | 31.6W | 31.6W |
| Drain Efficiency | 77% | 85% |
| Power Consumed | 41.0W | 37.2W |
| Power Dissipated | 9.4W | 5.6W |

Consistent small-signal gain contours indicate that correct S-parameters were correctly de-embedded from load pull data after each cut.




Outline




- Overview of approaches for improving efficiency at power back-off
- **Supply modulation**
 - GaN PA design (10GHz carrier)
 - Supply modulator (100MHz switching)
 - Integration and modeling
- Outphasing
 - Quasi-MMIC isolated and non-isolated
 - Measurements of load modulation internal to the PA
 - Outphasing with supply modulation
- Discussion and some other challenges



Supply-Modulated Transmitters

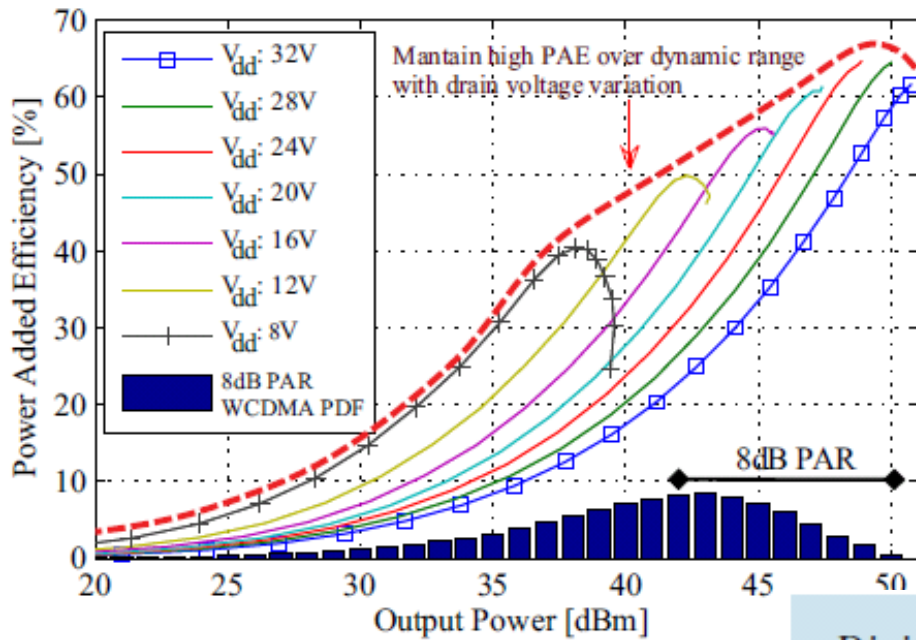
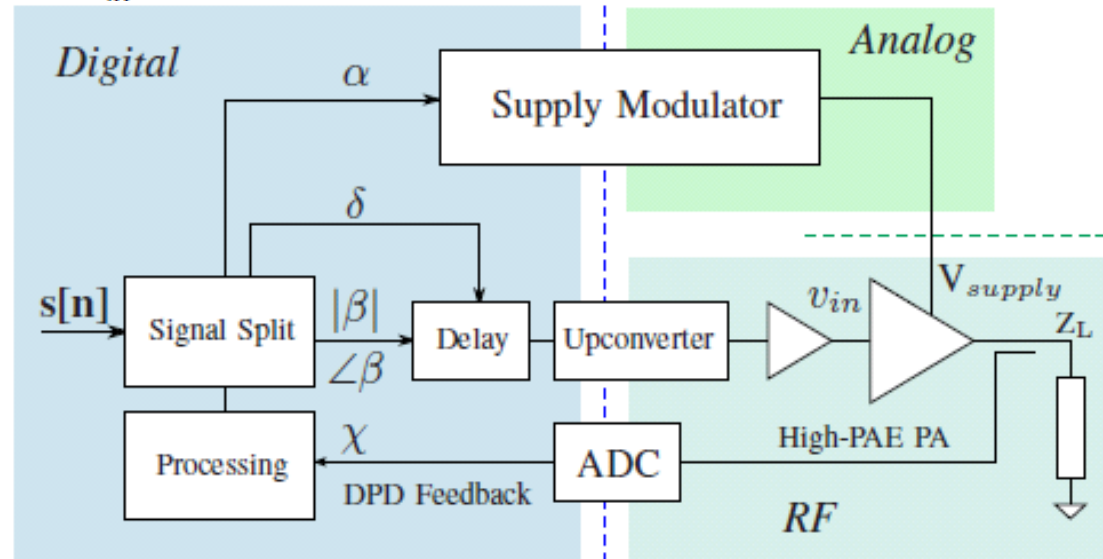
$$PAE = \frac{\int_0^{V_{max}} f_{PDF}(V) \cdot [P_{out}(V) - P_{in}(V)] dV}{\int_0^{V_{max}} f_{PDF}(V) \cdot P_{DC}(V) dV}$$





Components of SM-PA design




- **High-efficiency PA (e.g. harmonically-tuned)**
 - Improve maximum PA efficiency at a chosen power level with sufficient bandwidth for broadband signals
- **Efficient Supply Modulator**
 - Maintain PA efficiency at average power by varying the drain supply voltage
 - Enable high slew rates for tracking broadband signals
 - Introduce minimal reduction in overall efficiency
- **Linearization**
 - Restore linearity by identifying sources of distortion to simplify DPD
- **Integration and packaging**
 - Integrate supply modulator with PA with minimal loading
 - Thermal management
 - Integration of various drivers



High-Efficiency PA Design for SM



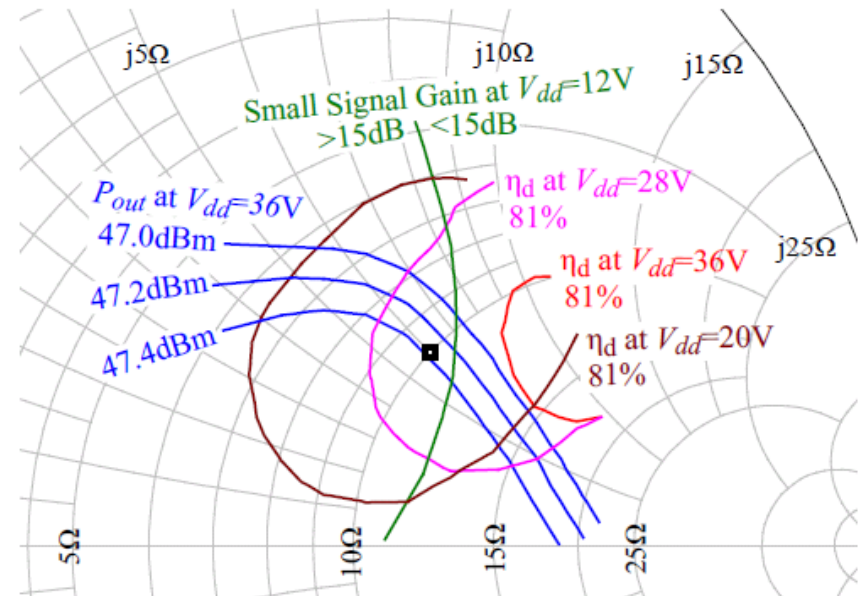- PA design has to take into account:
 - small signal gain
 - efficiency and
 - output power over a range of supply voltages corresponding to an input envelope range
- Use **TriQuint 0.15um GaN**:
 - 20V CW
 - 100um SiC substrate
 - 60um diameter vias
 - 240, 300 and 1200 pF/mm²
 - 50Ω/sq TaN resistors



| Parameter | Condition | Typical |
|-----------|---------------|-----------|
| IMAX | Vds = 20 V | 1.15 A/mm |
| Peak Gm | Vds = 20 V | 380 mS/mm |
| Vp | Ids = 1 mA/mm | -3.5 V |
| BVGD | Ig < 1mA/mm | 50 V |
| Ft | 20V-200mA/mm | 38 GHz |
| FMAX | 20V-200mA/mm | 140 GHz |



- Modeling:
 - Fit class Ab/B over a range of Vds
 - Pulsed IV at 25 and 85 deg C
 - S-parameters at 5, 10, 15, 20 V for Idq=10 and 100mA/mm
- Load pull PAE and power tuned at Vd=20V






High-Efficiency X-band MMIC PAs




Fixture

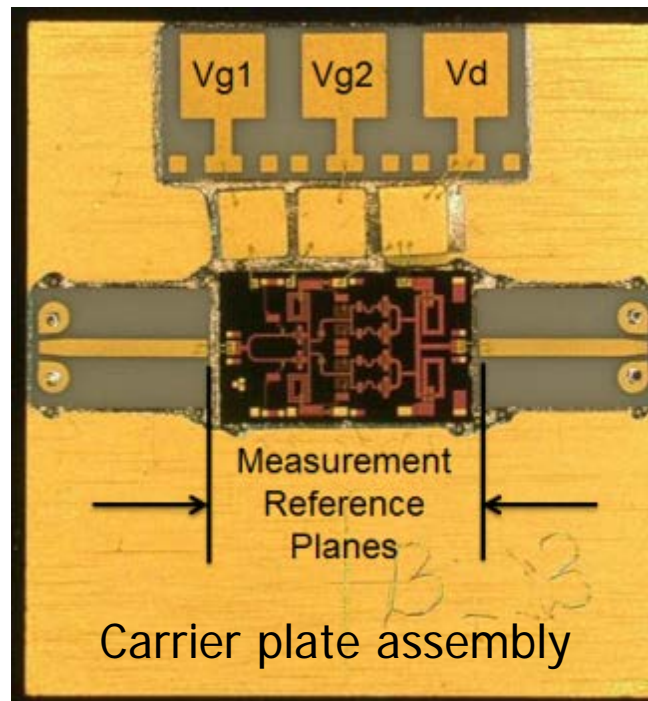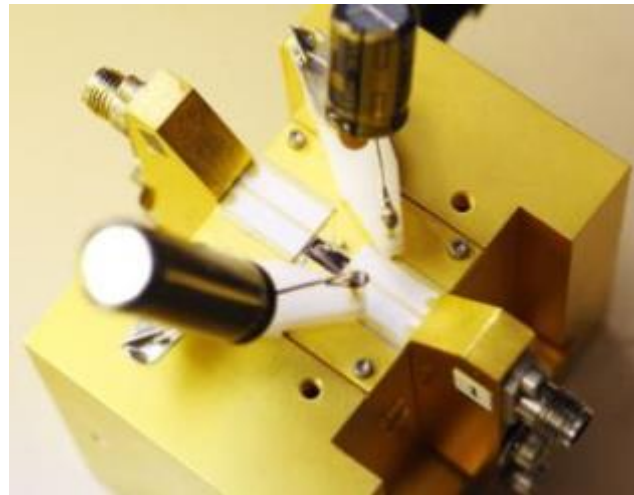


EM models for bondwires included in MMIC design

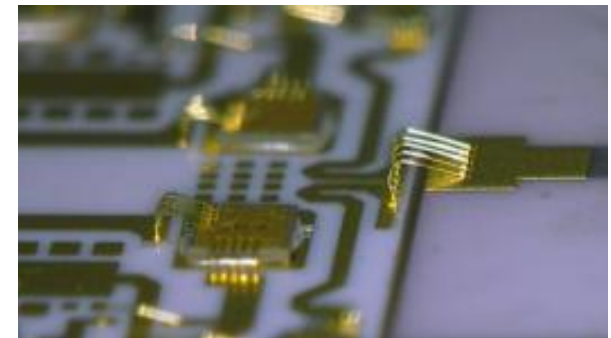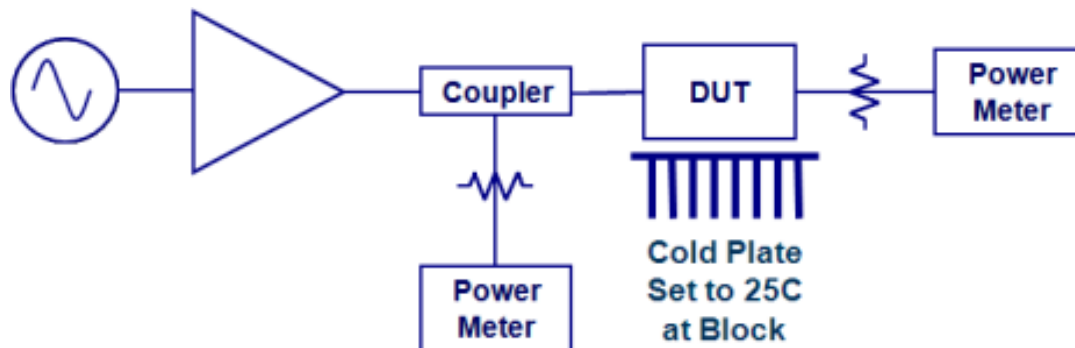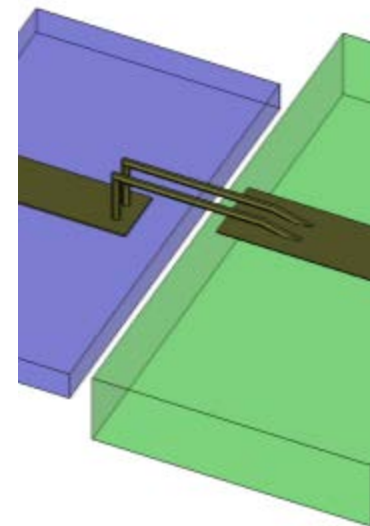


Example X-band MMICs

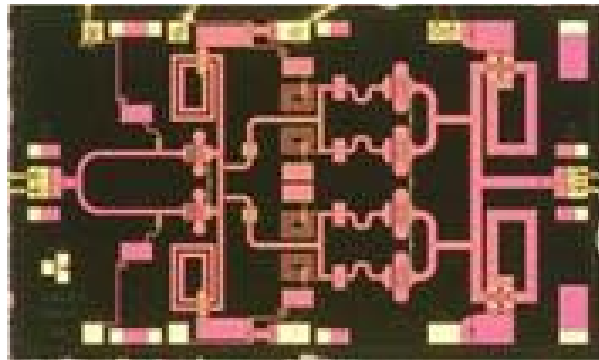


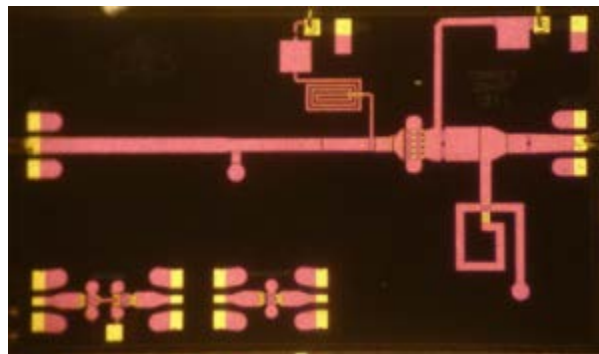
Circuit B:
2-Stage MMIC, combi
four 10x90um.
3.8mmx2.3mm



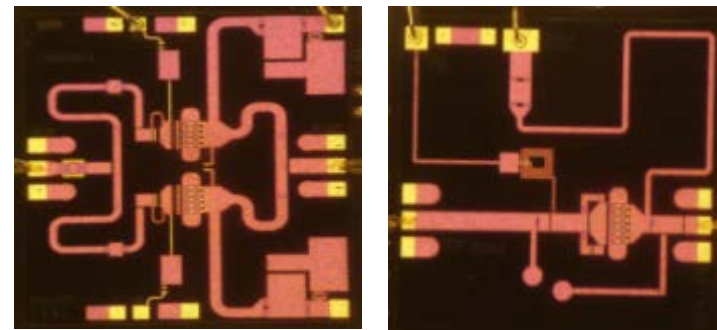Circuit F
Single stage, two
10x100um
2.0mmx2.3mm



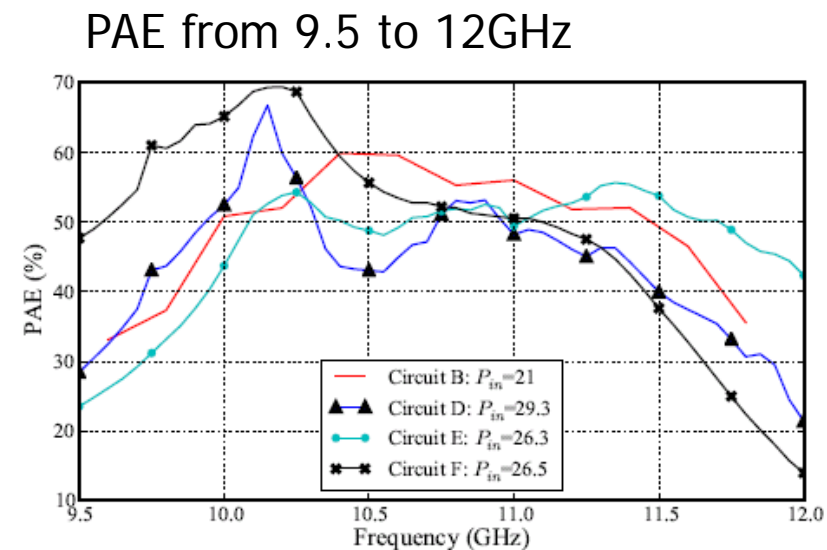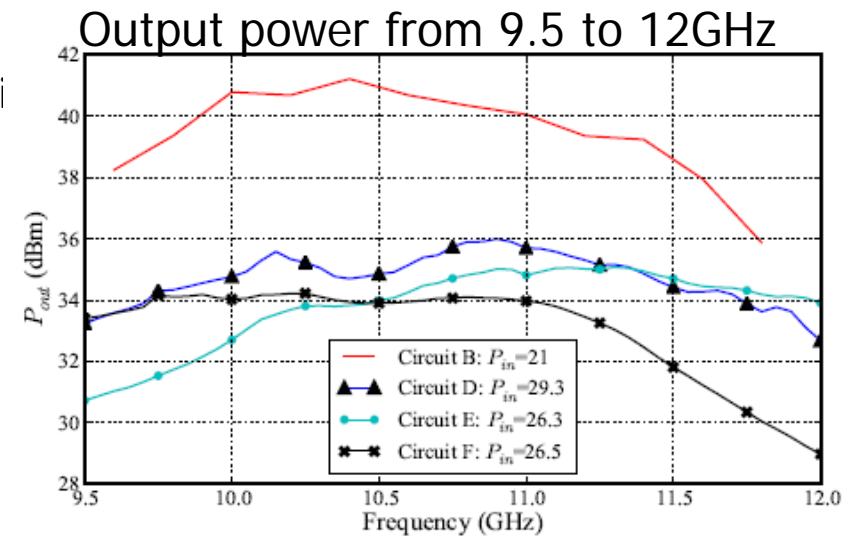Circuits D/ E
Single stage,
10x100um
3.8mmx2.3mm
and
12x100um
2.0mmx2.3mm







X-band MMICs for SM




| Circuit | B | D | E | F |
|---|---------|-------|-------|-------|
| Max PAE (%) | 59.9 | 66.8 | 55.7 | 69.4 |
| Max P_{out} (W) | 13.2 | 3.98 | 3.22 | 2.64 |
| Gate size (mm) | 3.6 | 2.0 | 1.2 | 1.0 |
| W/mm | 3.68 | 1.99 | 2.69 | 2.64 |
| BW at PAE=45% (GHz) | 1.6 | 0.77 | 1.88 | 1.95 |
| ΔP_{out} (dB) / ΔV_{ds} (V) | 11/12.5 | 3.3/7 | 4.8/9 | 5.3/8 |

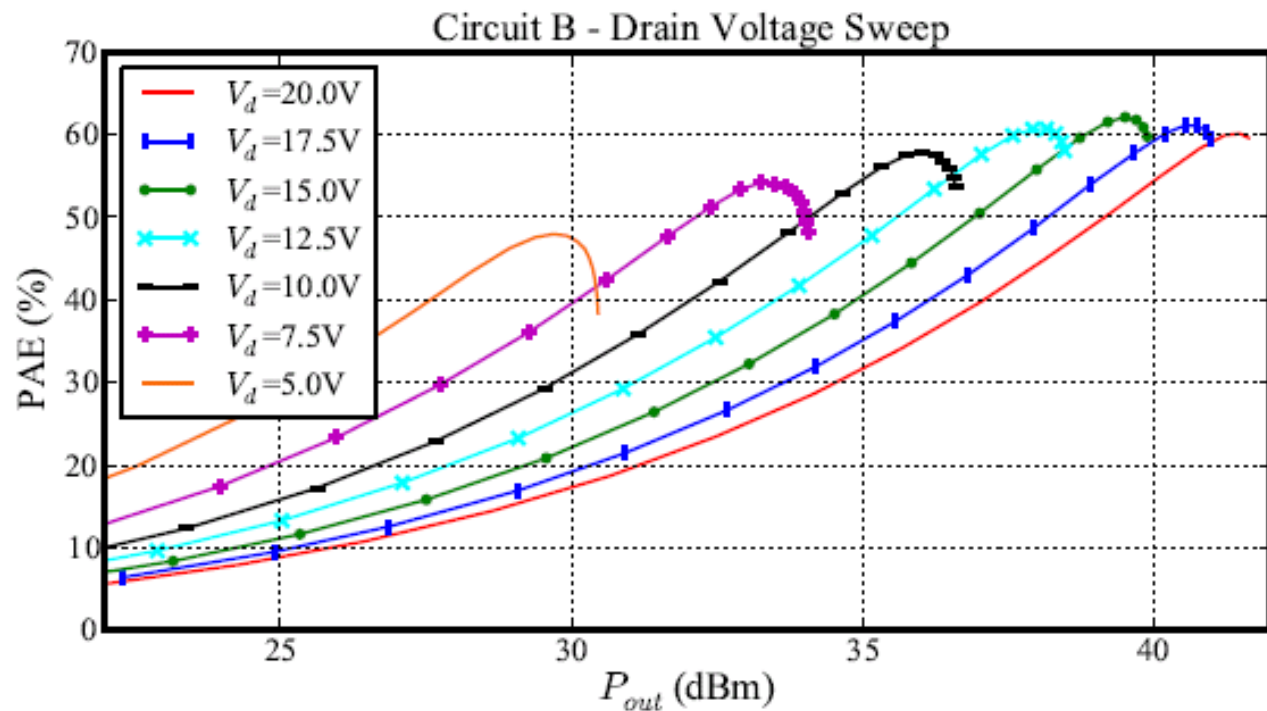
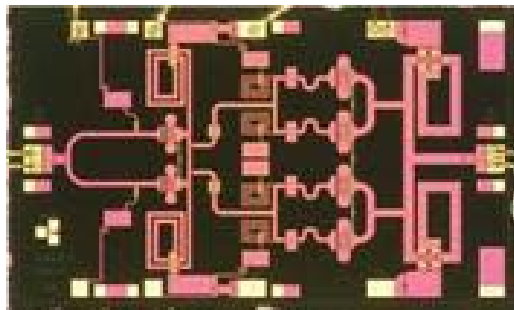





Some other MMIC PAs for SM

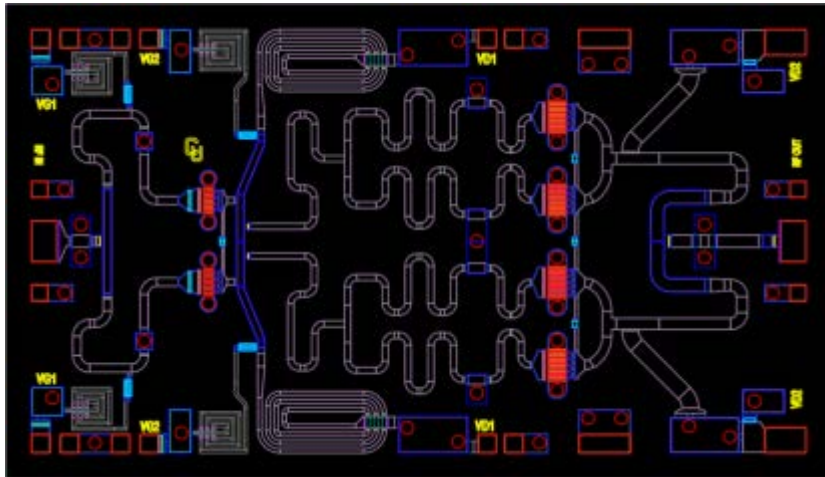

Run 2, $>10\text{W}$, more linear

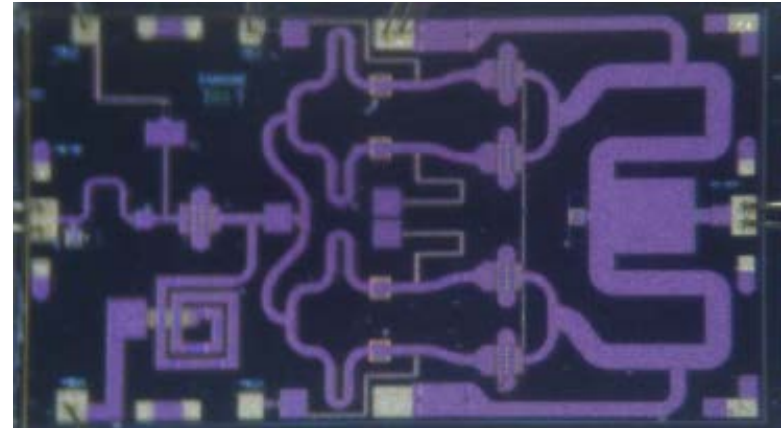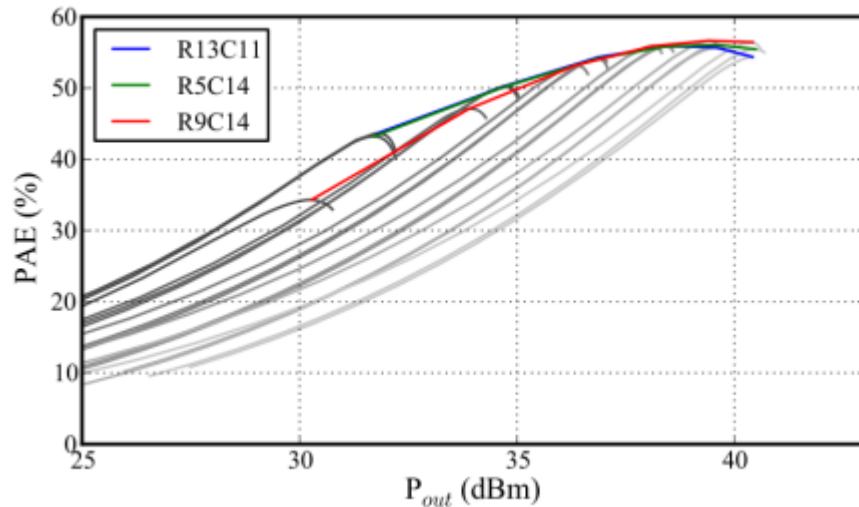

$>13\text{W}$, $>60\%$, $G=20\text{dB}$

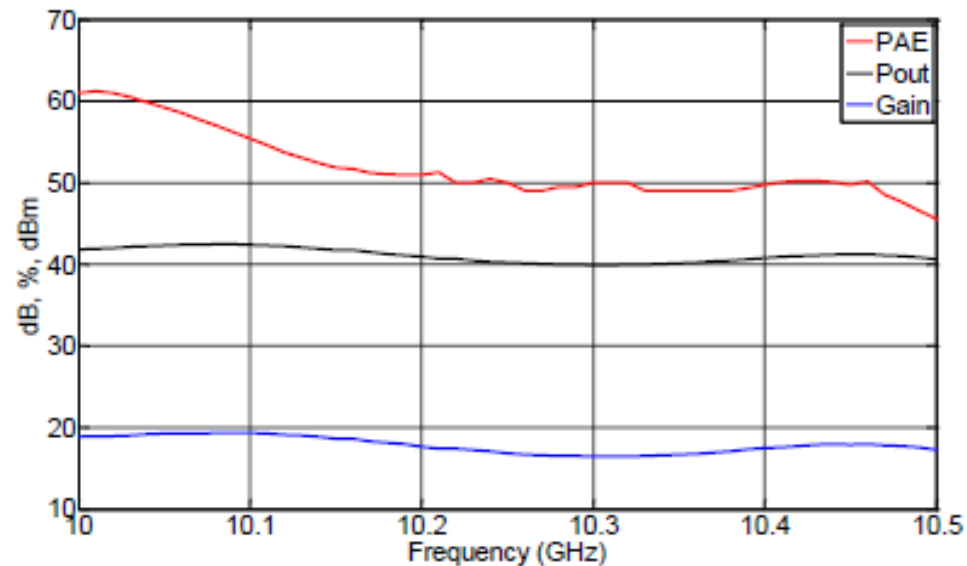






Real signal, integrated transmitter




- $G = 18\text{dB}$ (constant)
- Both stages supply-modulated
- For reasonable AM/AM, 11V of voltage dynamic of the drain supply
- At low V_{dd} , gain drops
- Increasing gate bias voltage may improve the achievable dynamic range

PA MMIC EG0490A, two stages, 10W

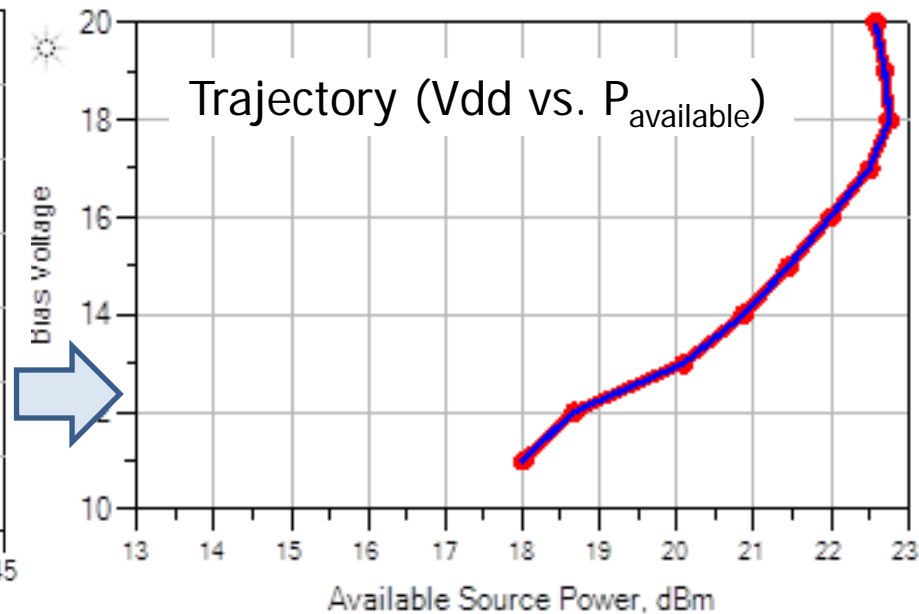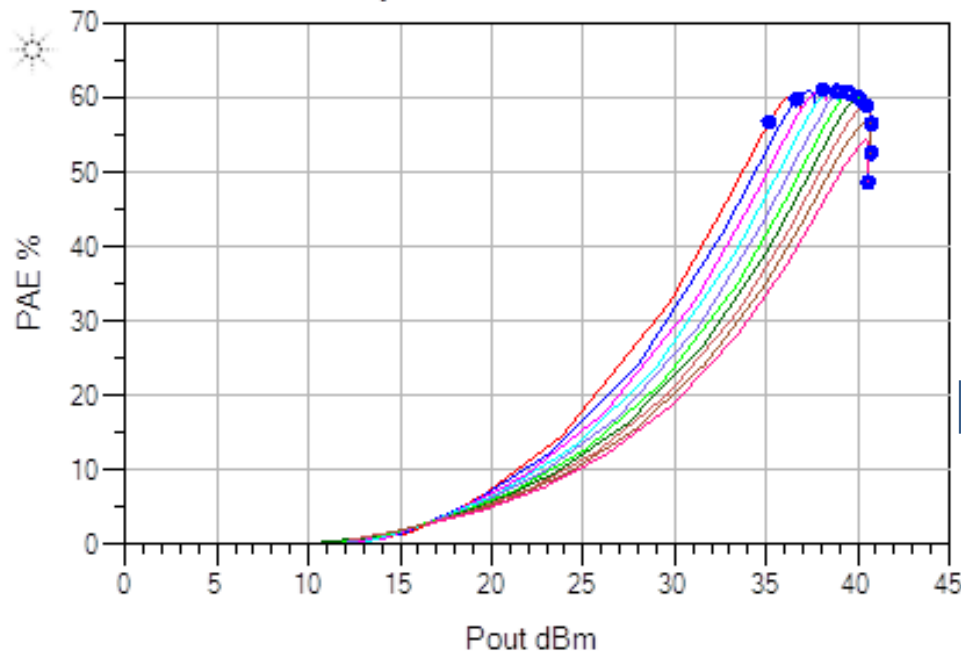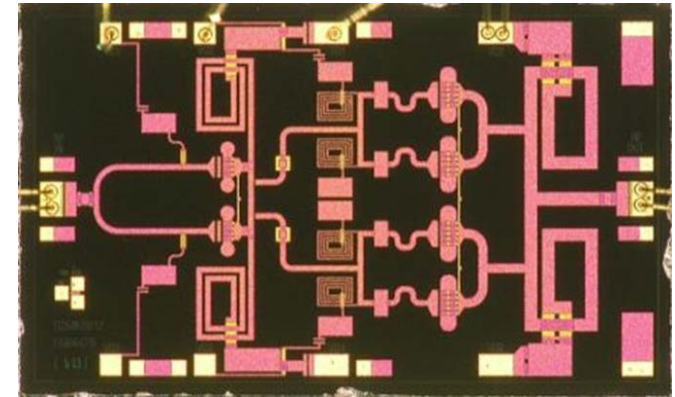



Measured vs. simulated static PA

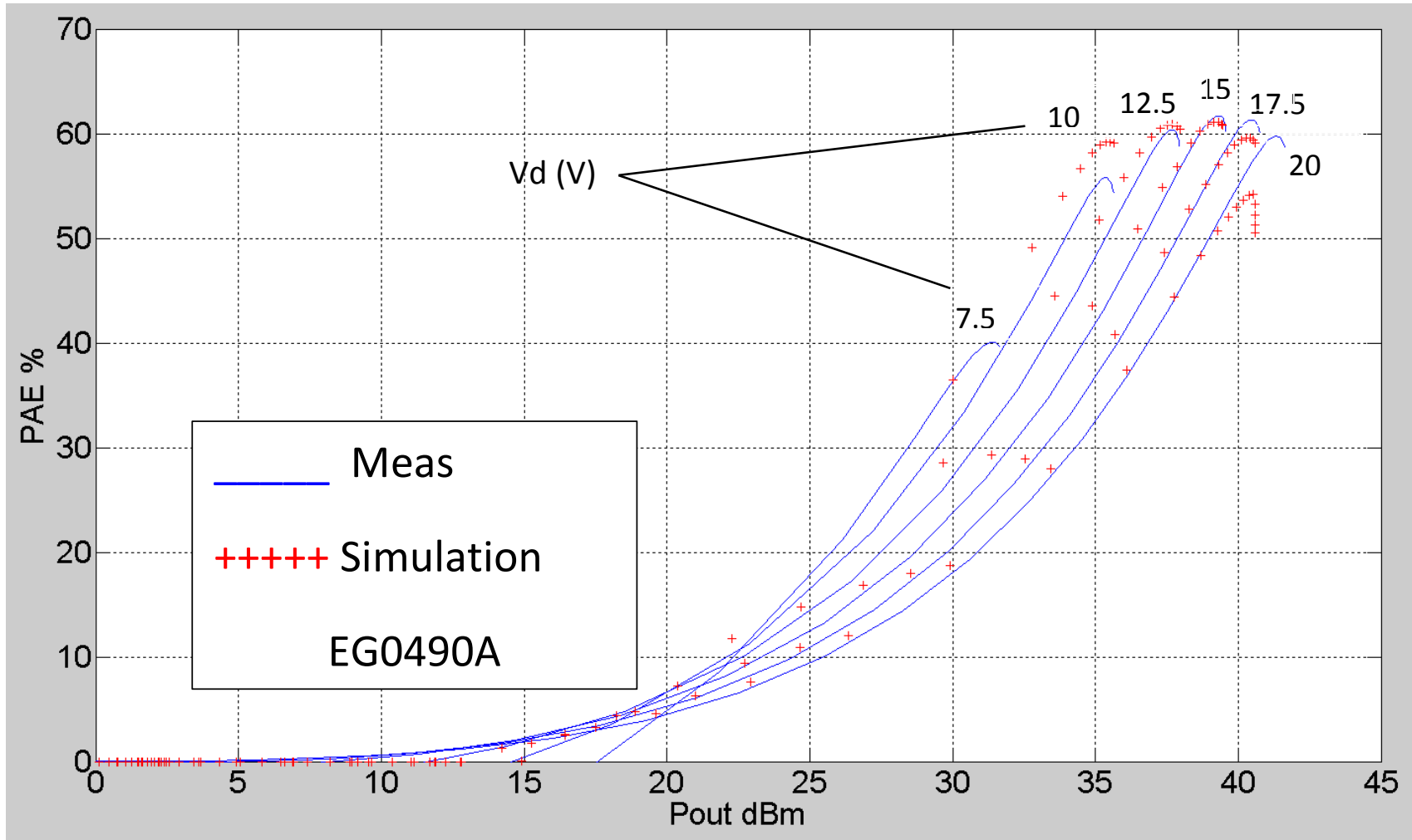




Signal characteristics




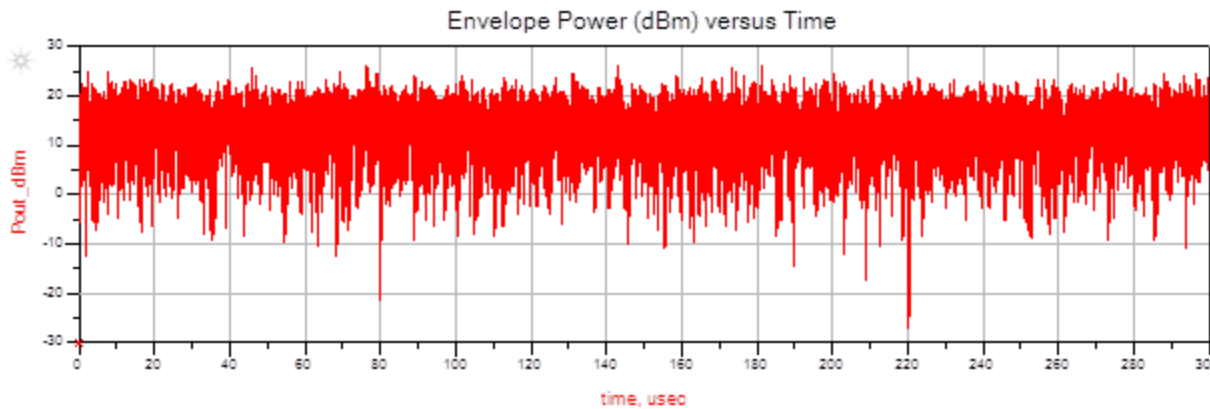
Example: LTE 18MHz 3GPP standard signal, envelope transient simulation




Envelope in time domain
Average power 16dBm

CCDF

Spectrum

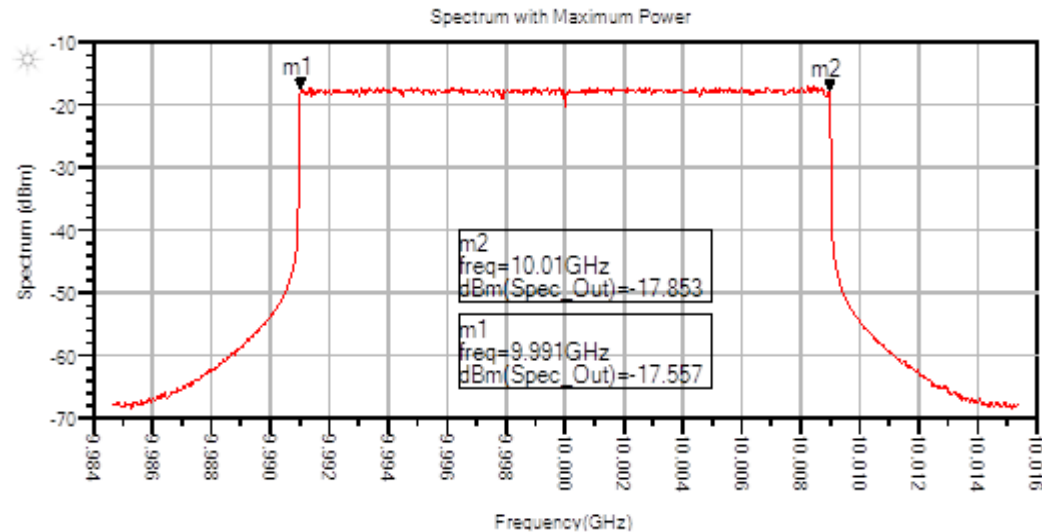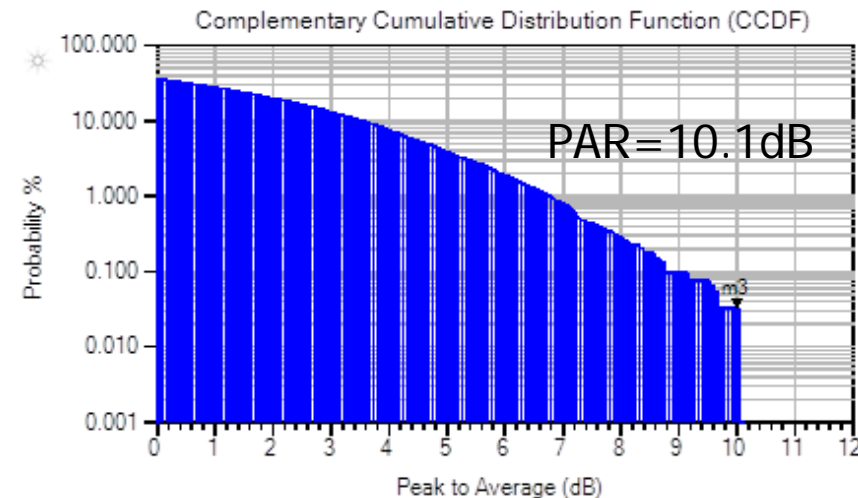


GaN supply modulator

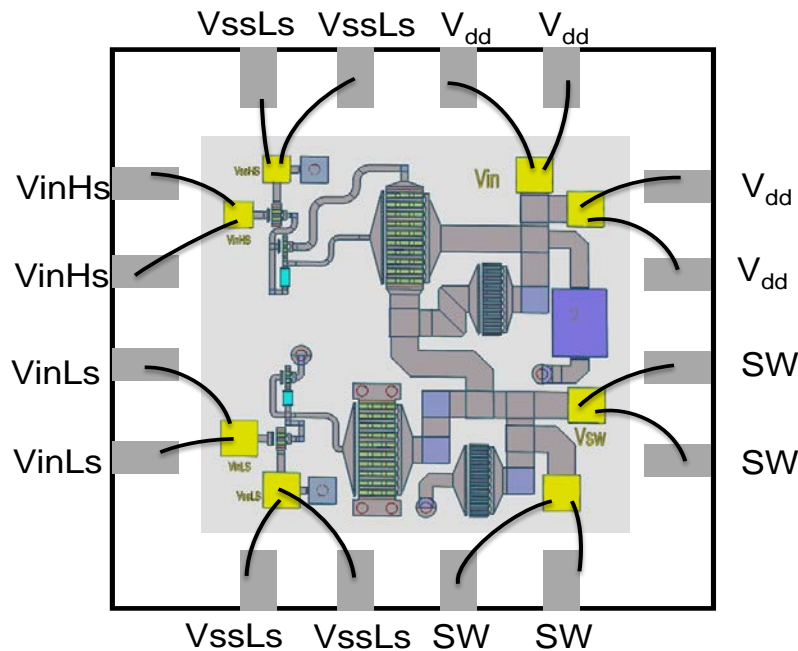

The switching converter operates as expected, showing an output voltage waveform ranging from 0V to 19V


The high state of the PWM signal does not reach 20V because of the on resistance of the transistor.

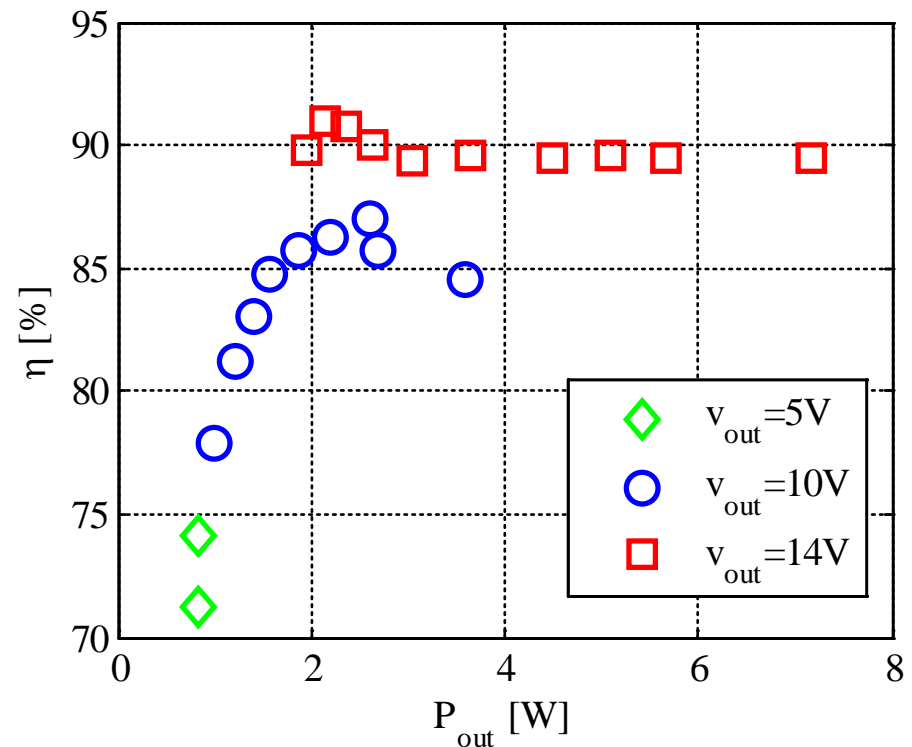150-nm GaCN on SiC MMIC
Standard QFN package
10W at 20V, 100MHz switching





Measured vs. simulated DSM

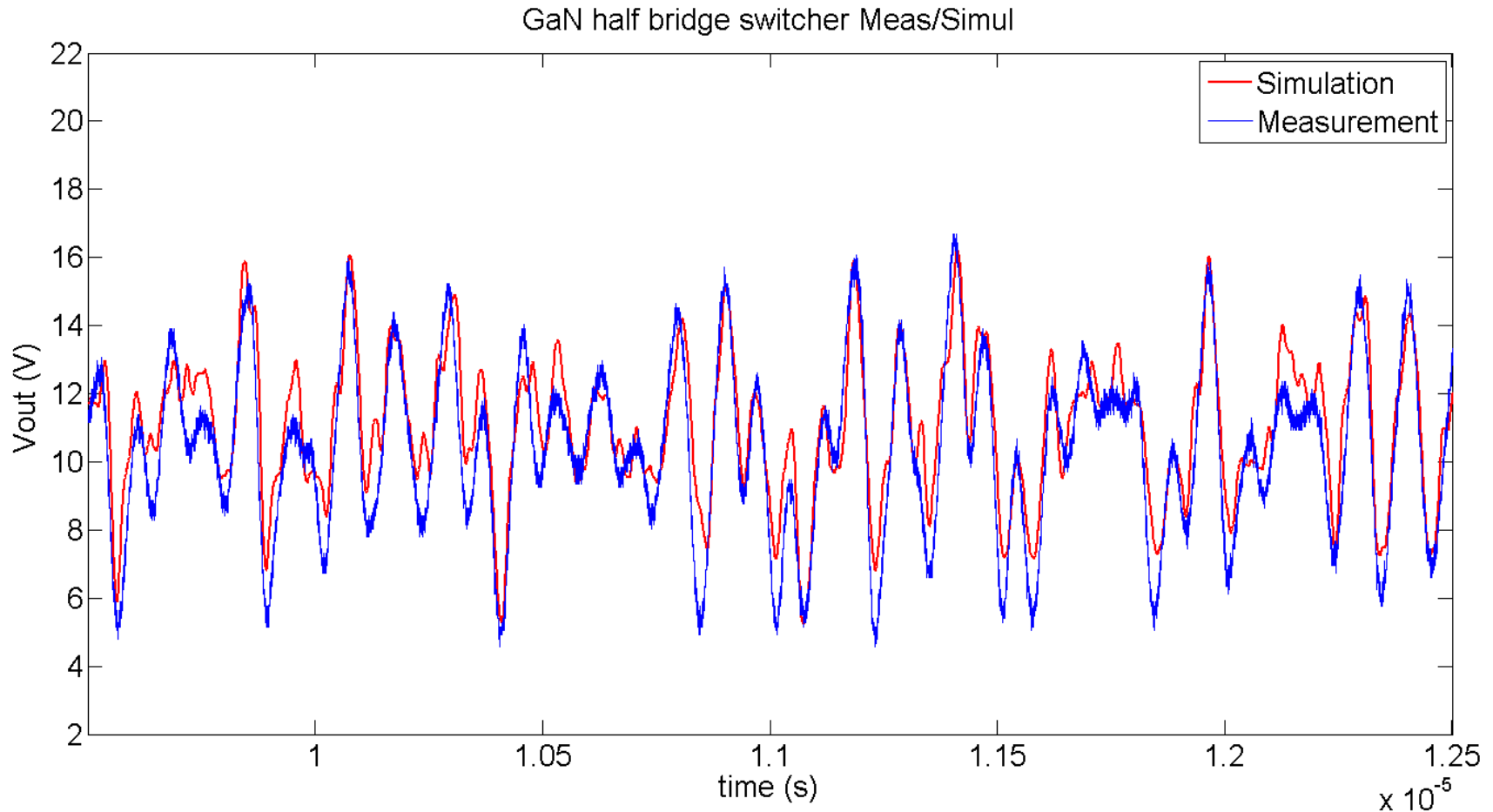

$$RMS\ error = 100 \times \sqrt{\frac{\sum_{t=1}^n (V_{out,t} - V_{in,t})^2}{n}} \times \frac{1}{(V_{out_max} - V_{out_min})} = 4.5\%$$





Issues for SM-PA design



- PA Supply Sensitivity:

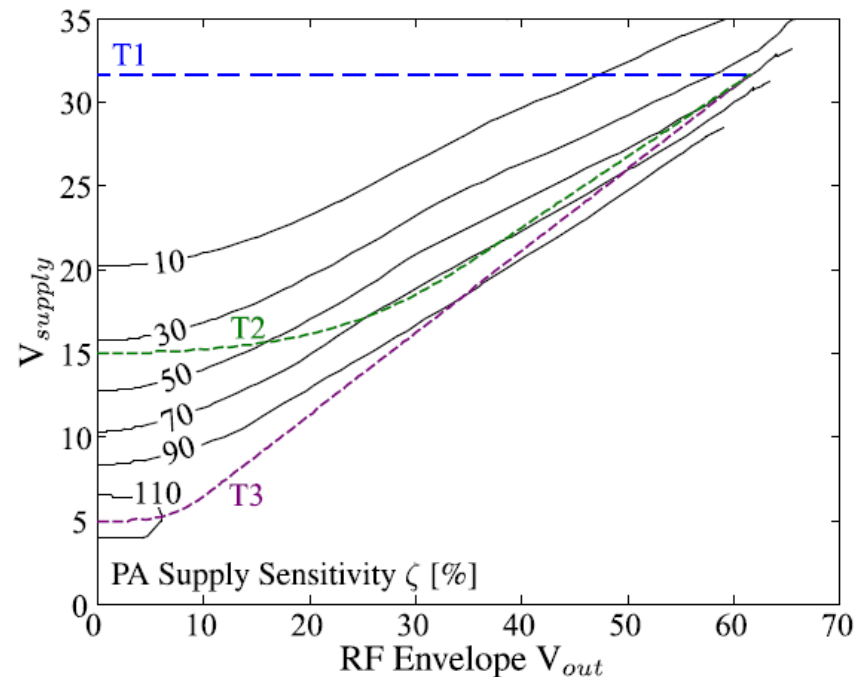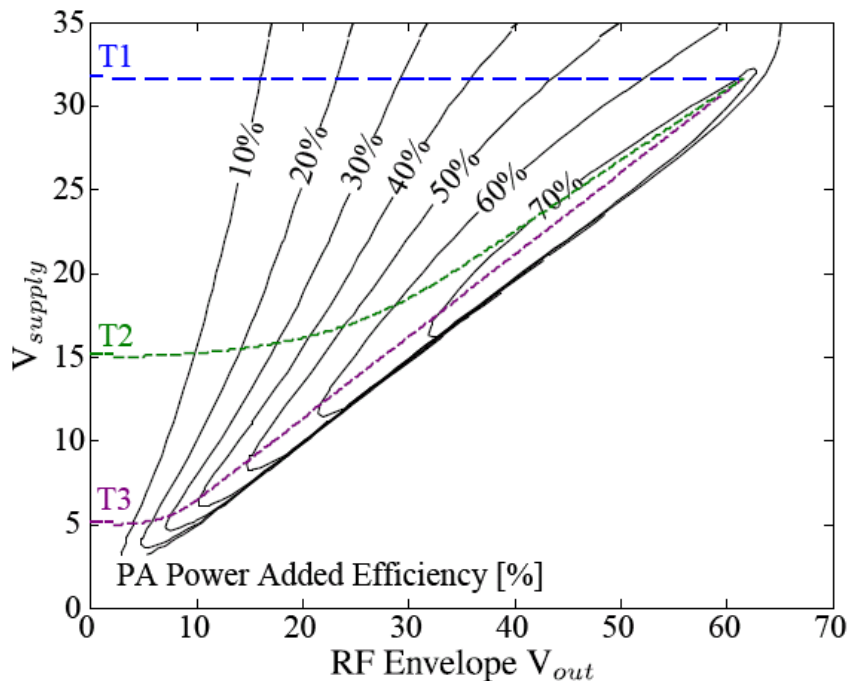
$$\zeta = \frac{\frac{\Delta V_{out}}{V_{out}}}{\frac{\Delta V_{supply}}{V_{supply}}} \times 100\%$$



- High slew rate (envelope signal bandwidth)
- Dynamic drain complex impedance loads supply modulator




PA performance with LTE signal

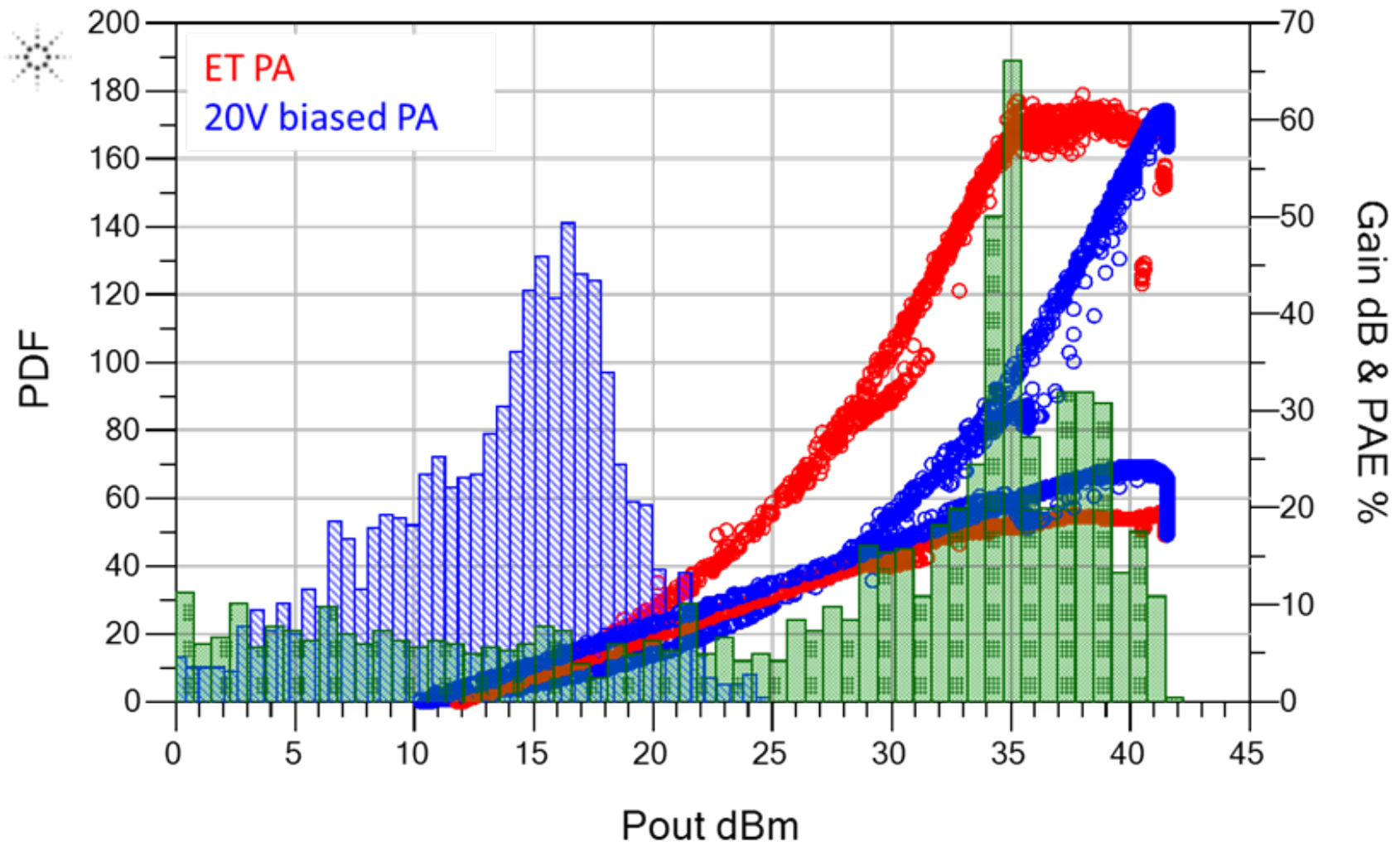





Test bench

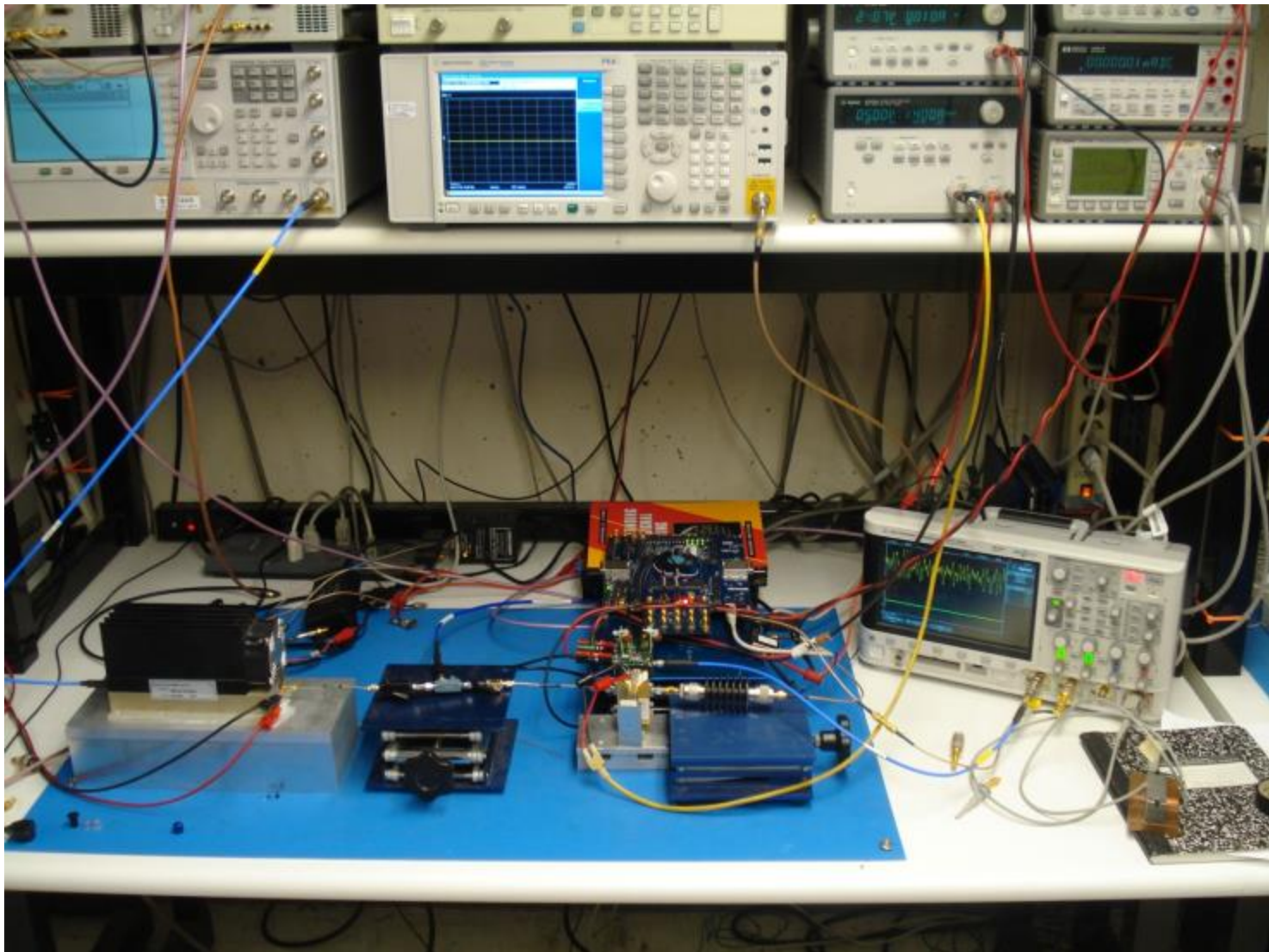



Example measured results

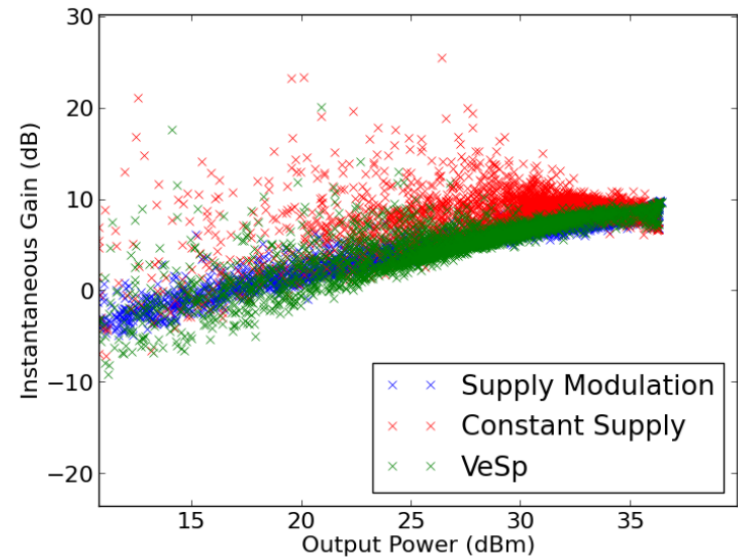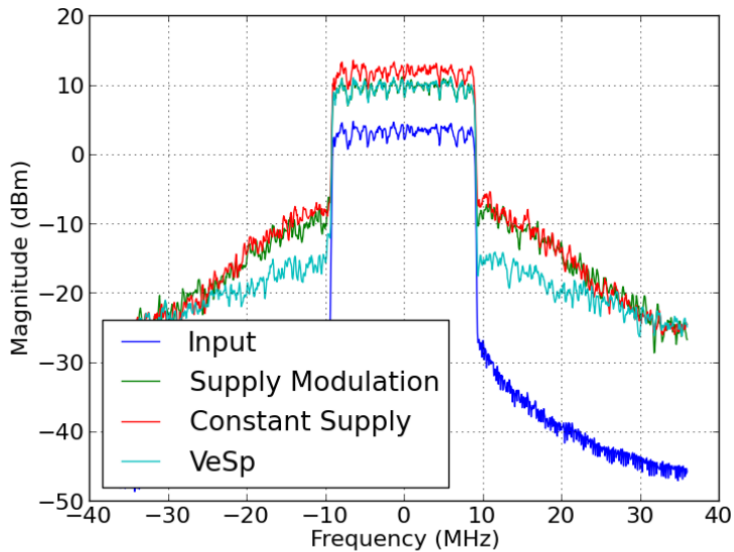


18MHz LTE
PAR=7.1dB

| | Constant Supply | Modulated Supply | VeSP |
|---------------|-----------------|------------------|------------------|
| Channel Power | 30.6 dBm | 28.6 dBm | 28.5 dBm |
| Peak Power | 36.3 dBm | 36.5 dBm | 36.5 dBm |
| CPAE | 43.9% | 65.4% (34.8%) | 62.6% (33.1%) |
| Current | 108.0 mA | 75.6 mA | 80.2 mA |
| ACPR | -27.1 dB | -23.3 dB | -28.0 dB |
| EVM | -31.2 dB | -29.3 dB | -29.3 dB |




High-bandwidth SM-PAs

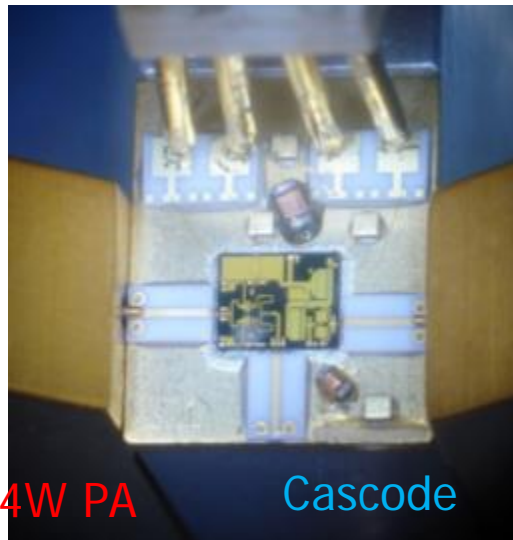

4W PA


Cascode

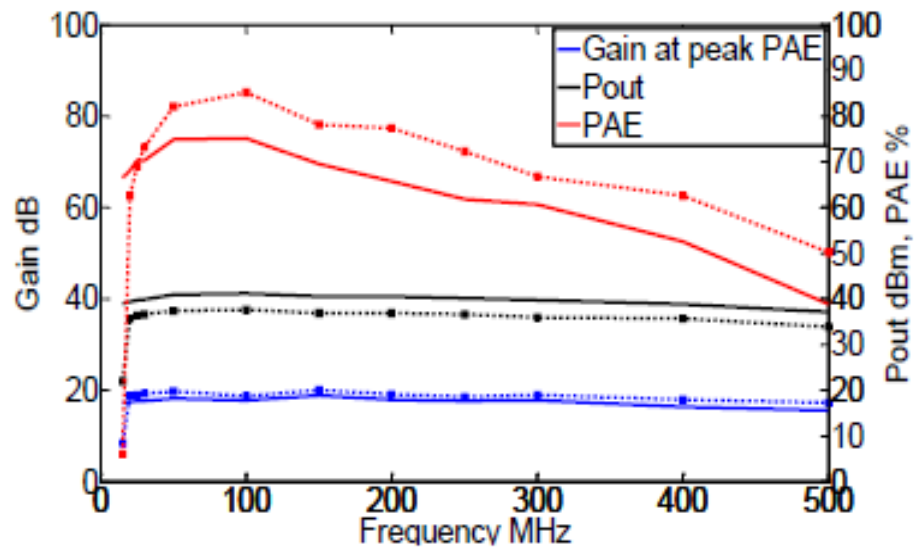


RF envelope input

Cascode VHF PA

DC + RF pads

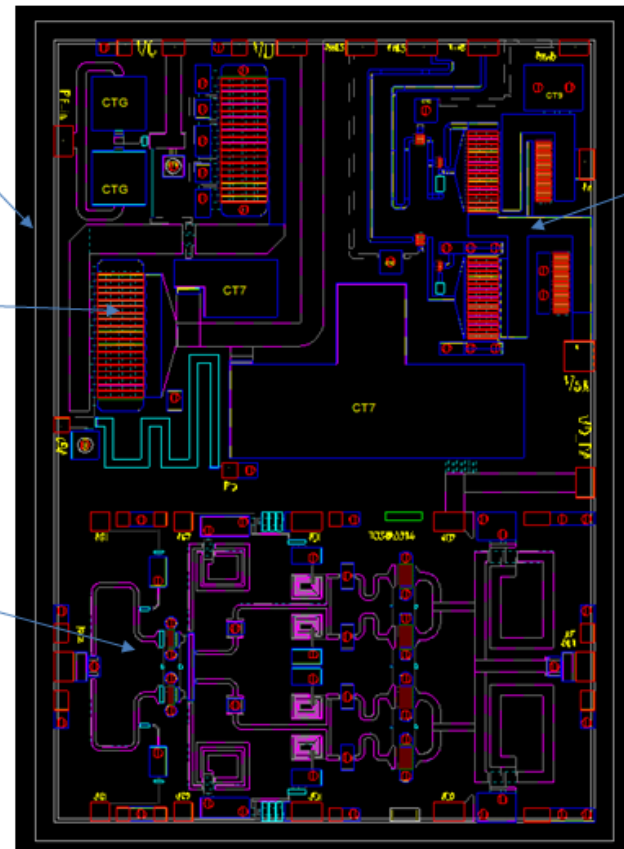

Single-phase half bridge converter

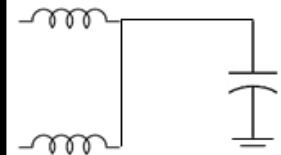

Off chip filtering

- Higher band: 15-500MHz 80%-50%
- Lower band: 90% efficiency, >5W, 100 MHz switching




Outline



- Overview of approaches for improving efficiency at power back-off
- Supply modulation
 - GaN PA design (10GHz carrier)
 - Supply modulator (100MHz switching)
 - Integration and modeling
- **Outphasing**
 - Quasi-MMIC isolated and non-isolated
 - Measurements of load modulation internal to the PA
 - Outphasing with supply modulation
- Discussion and some other challenges





Quasi-MMIC outphasing PA

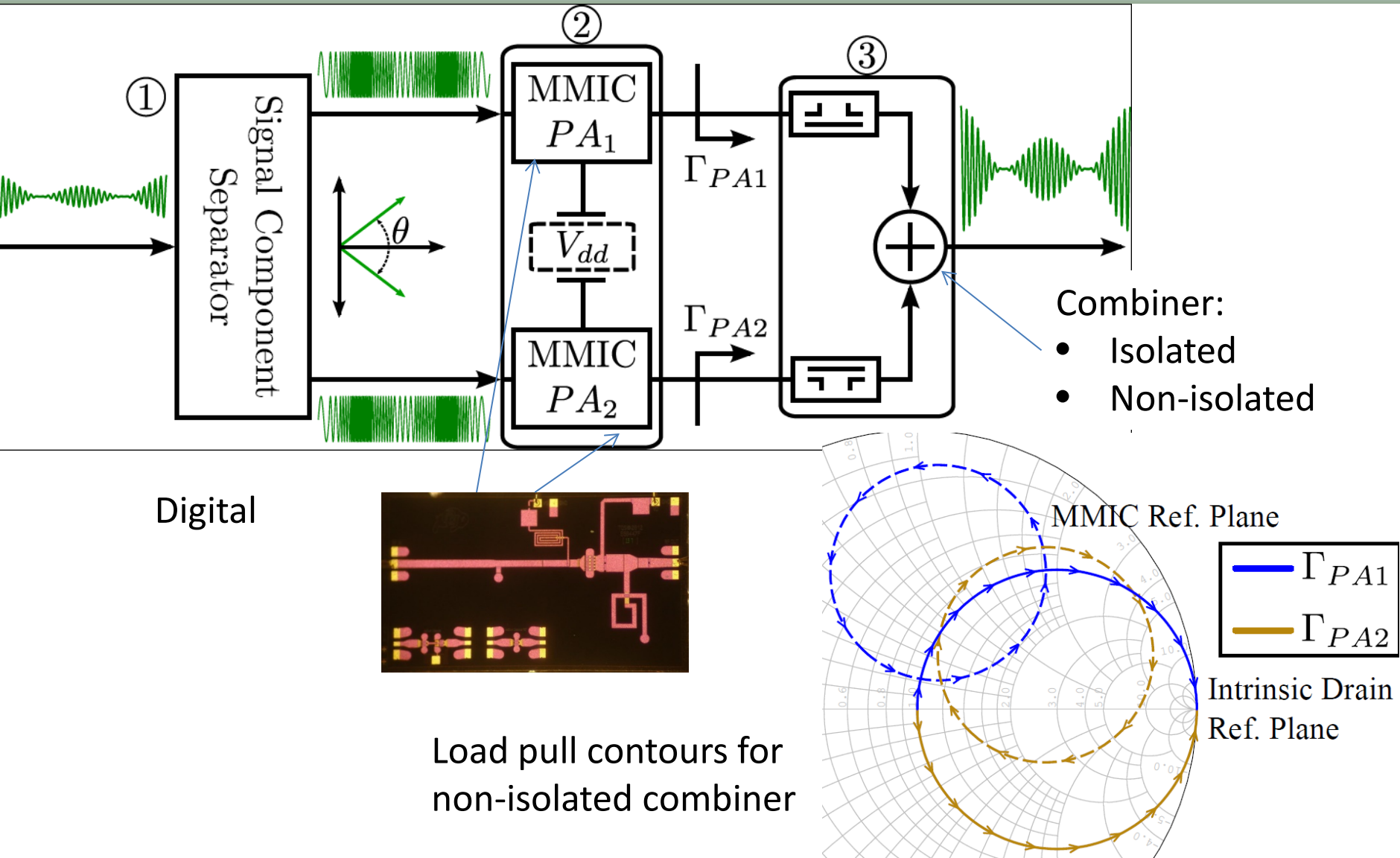



PA element for outphasing PAs

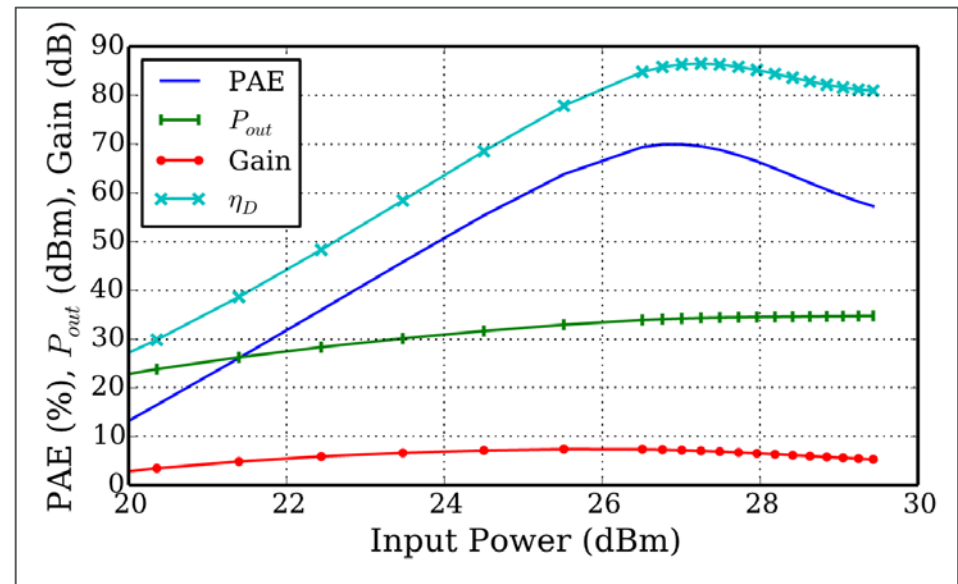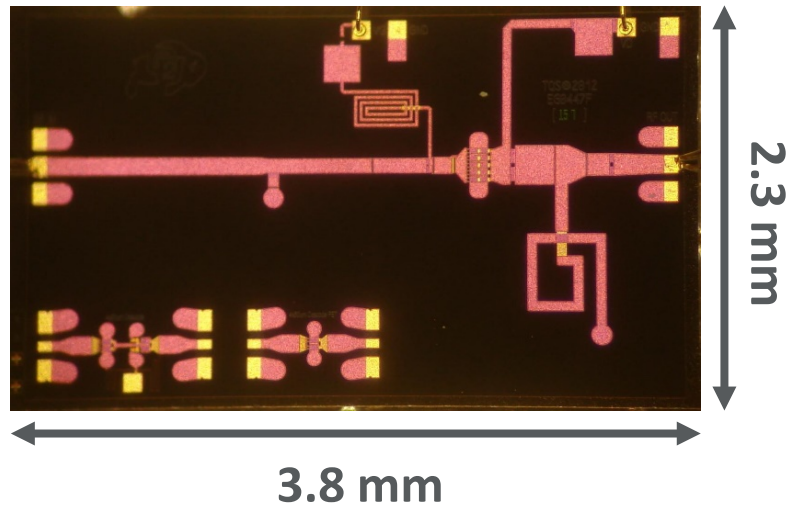


- Single-stage
- Biased in class-B
- GaN MMIC PA (TriQuint 0.15 μm)
- 10 x 100 μm FET


- $V_{DD} = 20 \text{ V}$, $V_G = -4.0 \text{ V}$
- $f_0 = 10.1 \text{ GHz}$
- Peak PAE = 70%
- $P_{out} = 2.7 \text{ W}$
- Gain = 7.2 dB



Isolated combiner


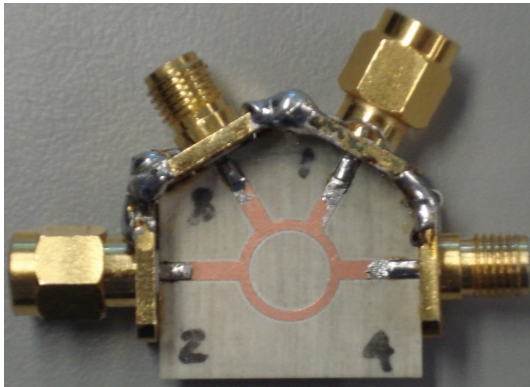


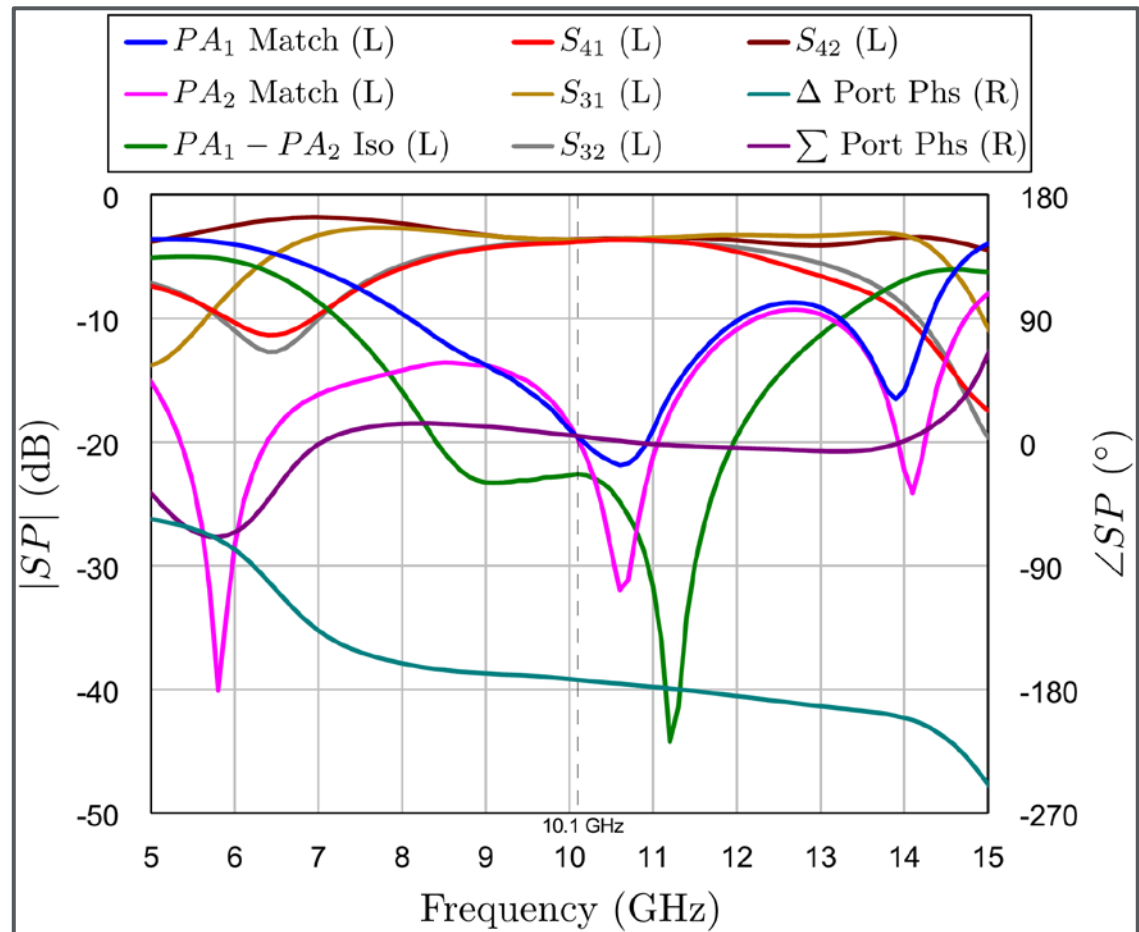- 180° rat-race
- 30 mil Ro4350B
- < 1.4 dB loss
- 22.5 dB isolation
- > 19.5 dB return loss



- 4.5° sum port phase
- 173° diff port phase


Non-isolated Combiner

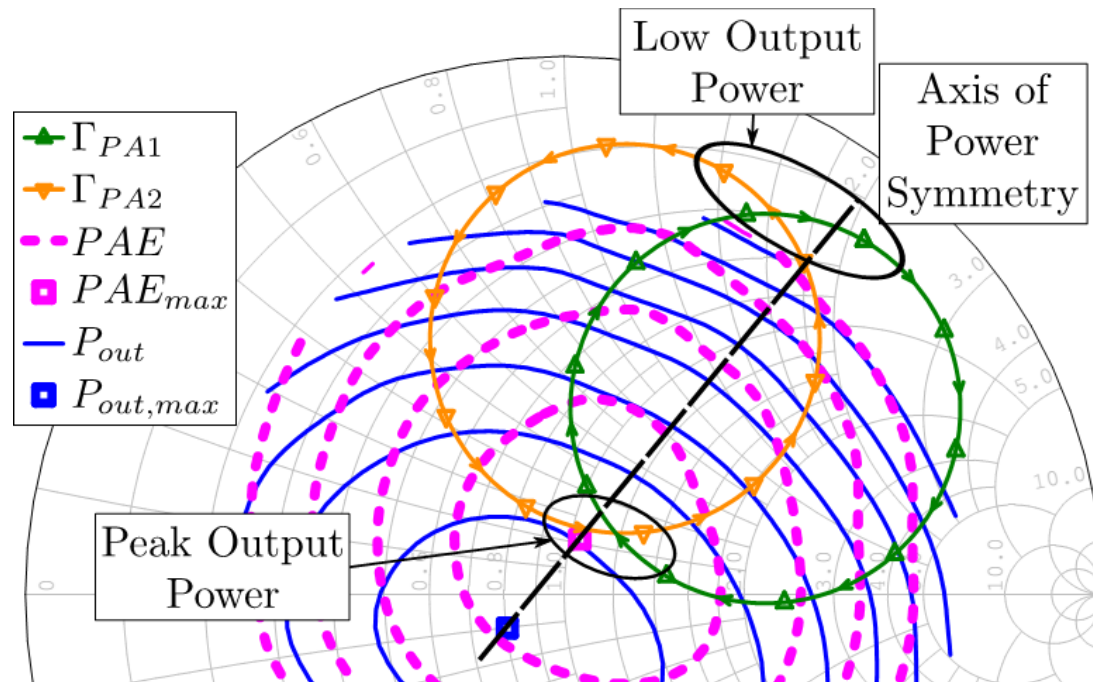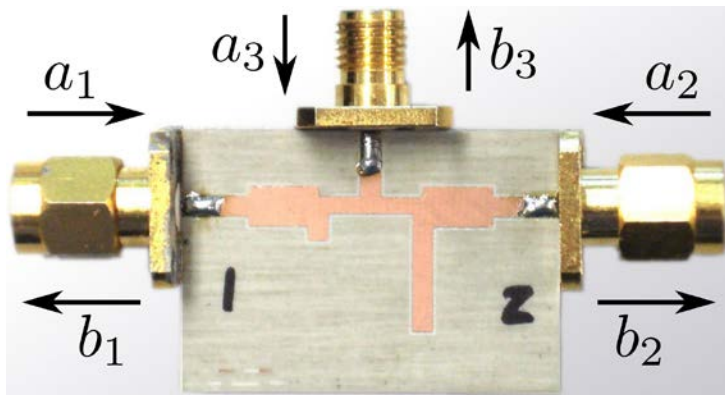

- Shunt susceptances and tuned 90° TLs
- Load modulation intersects at peak PAE load
- Internal PA power balance reasonably maintained





Internal PA Load Modulation

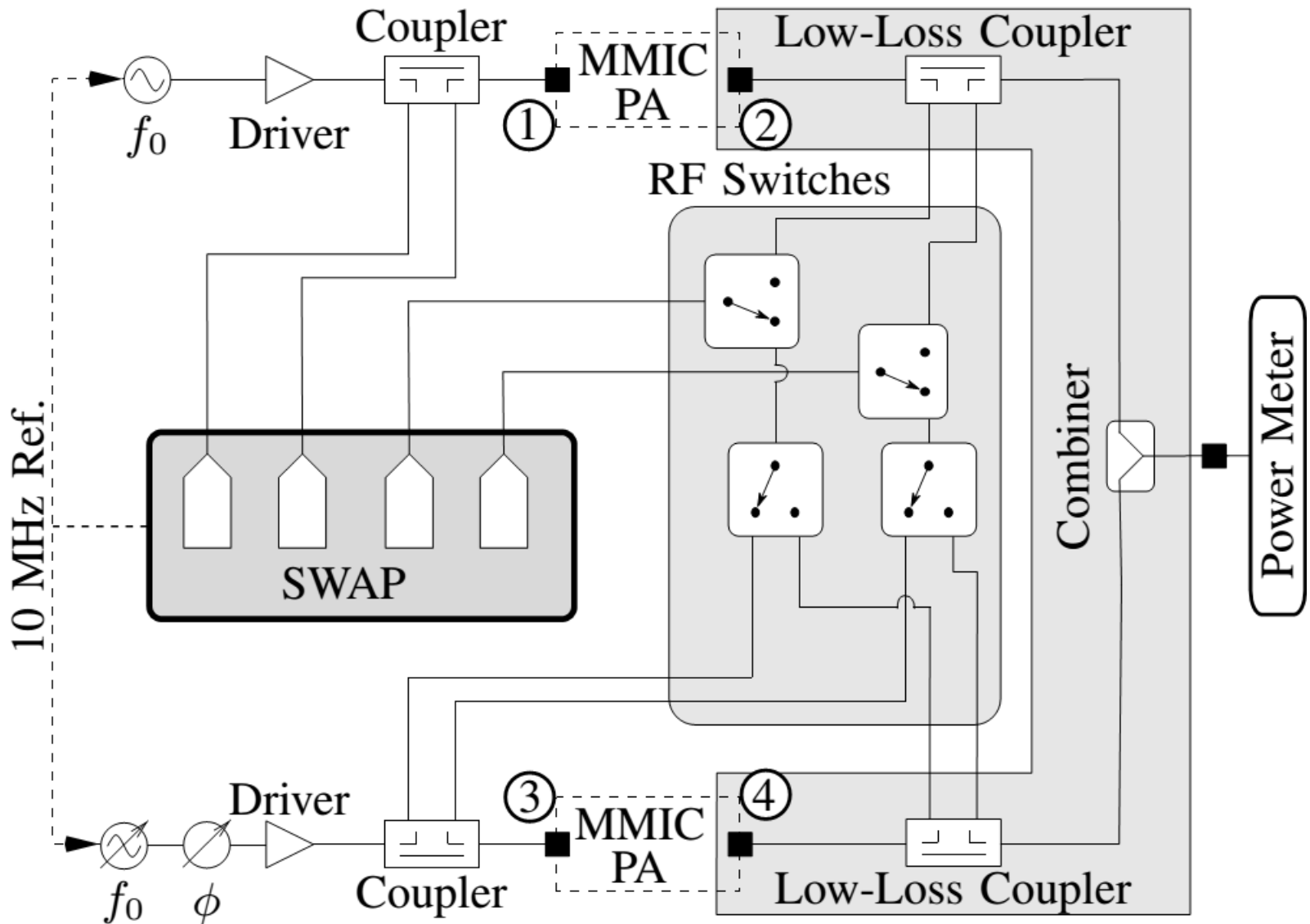





Isolated Outphasing PA

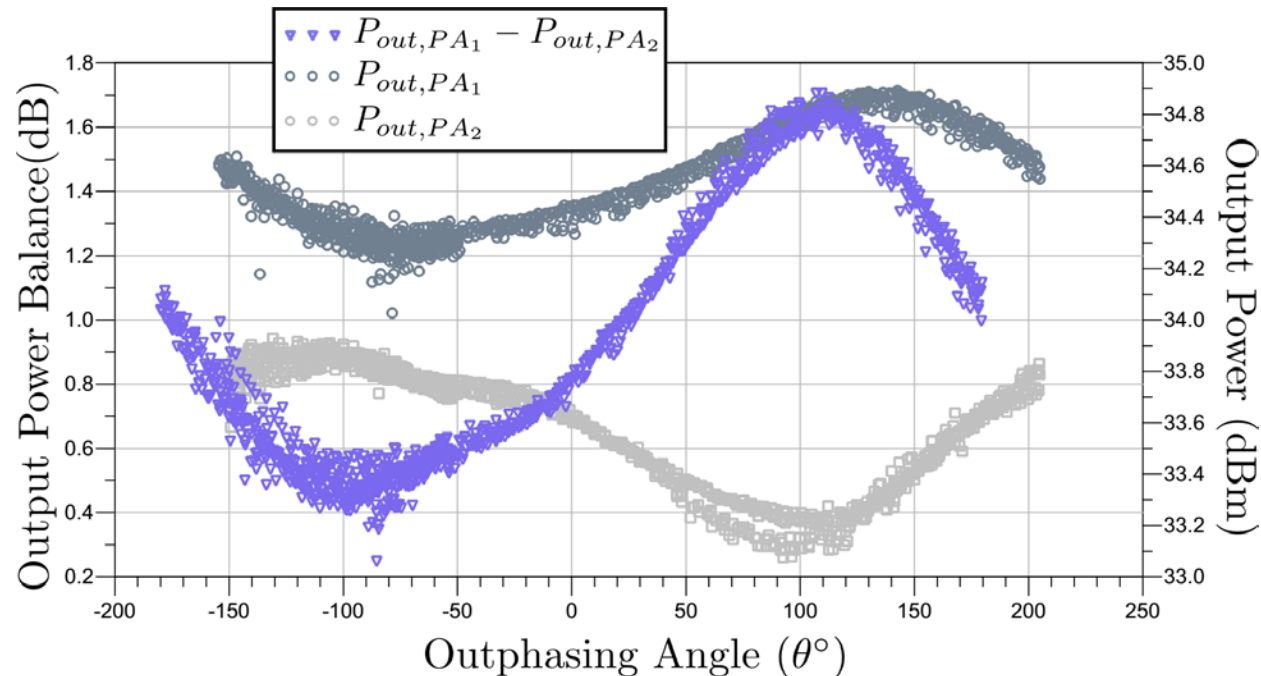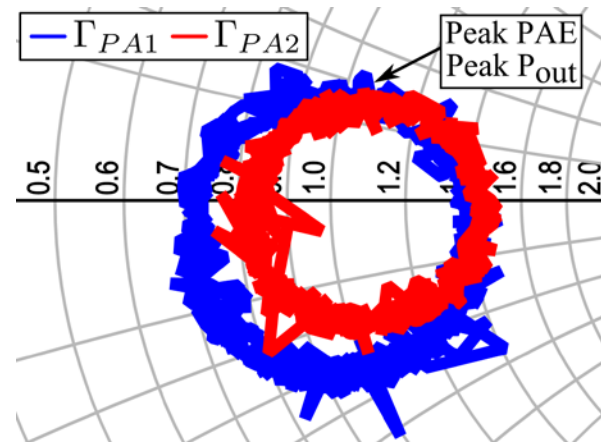

- Finite isolation yields minimal load modulation
- PAs rotate in opposite direction around contours
- 0.4 – 1.7 dB internal PA P_{out} imbalance caused by varying load



Non-Isolated Outphasing PA

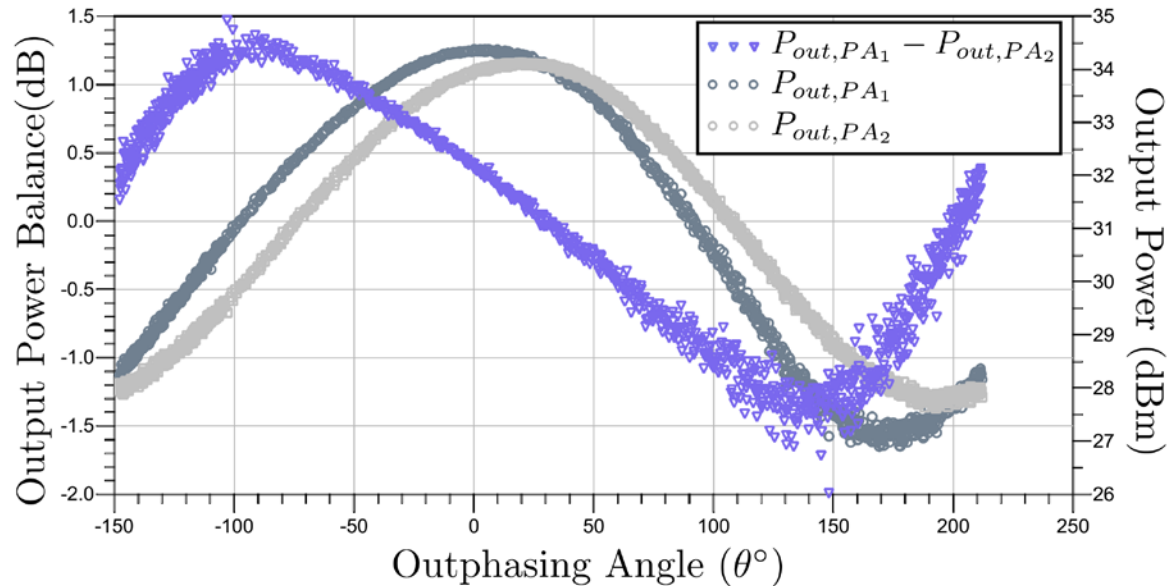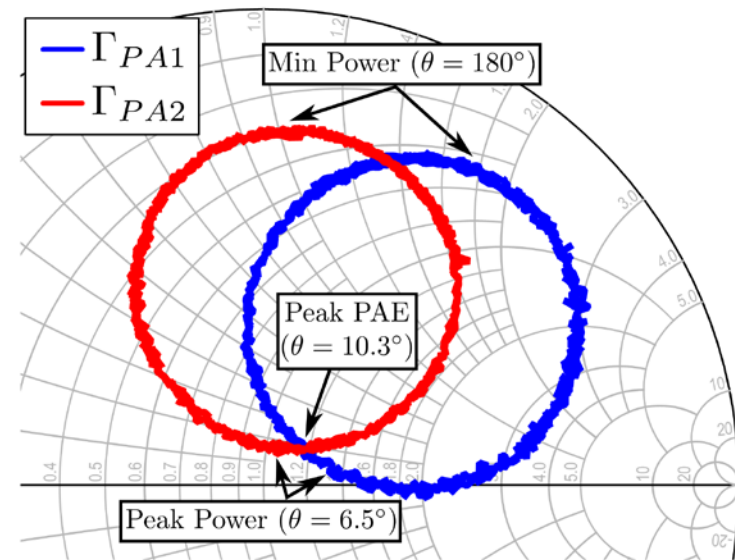


- Load modulation shows slight CW rotation due to ± 1.5 dB internal PA Pout imbalance
- Peak power occurs near peak PAE
- Minimum Pout of 3.6 dBm near edge of smith chart



Comparison




Isolated

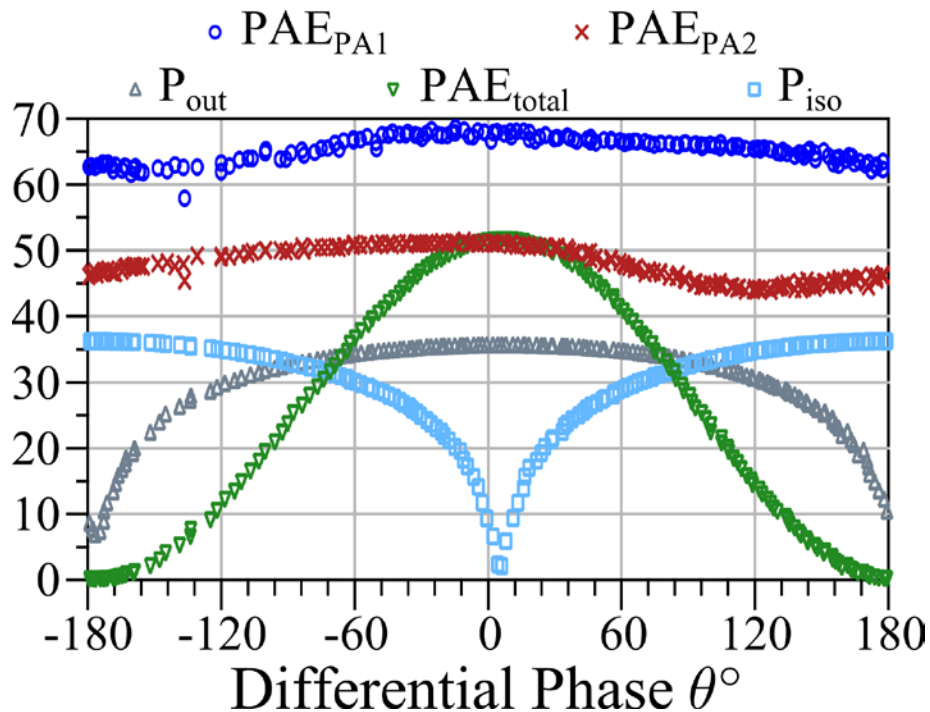

- Peak P_{out} = 35.8 dBm / 36.8 dBm
- Peak PAE = 41.6 % / 59%
- Integrated design: 1 dB less loss



Non-isolated

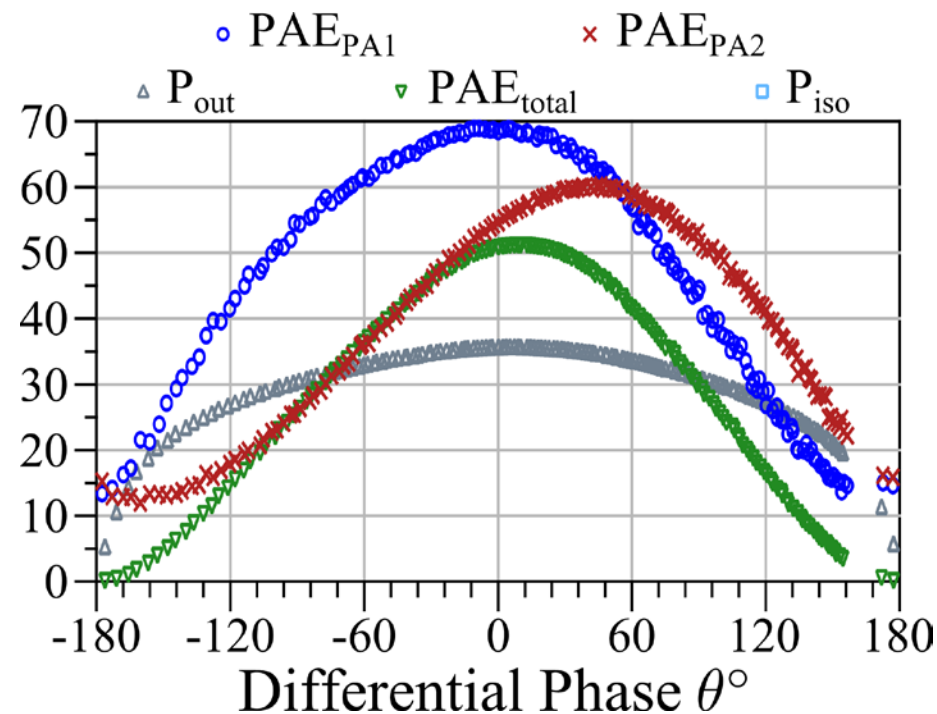

- Peak P_{out} = 35.7 dBm / 37 dBm
- Peak PAE = 41.5 % / 60% (L=1.3 dB)
- 8 % improvement in PAE at 4 dB OPBO



Effect of Power Unbalance

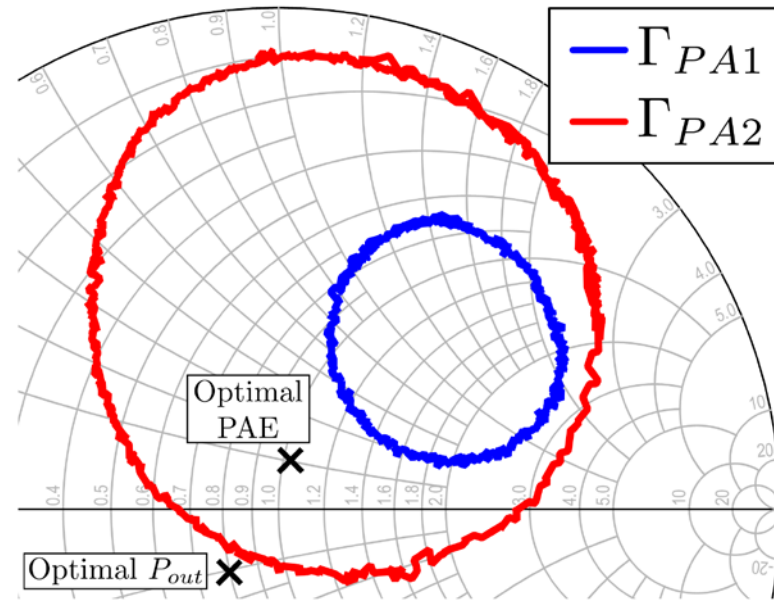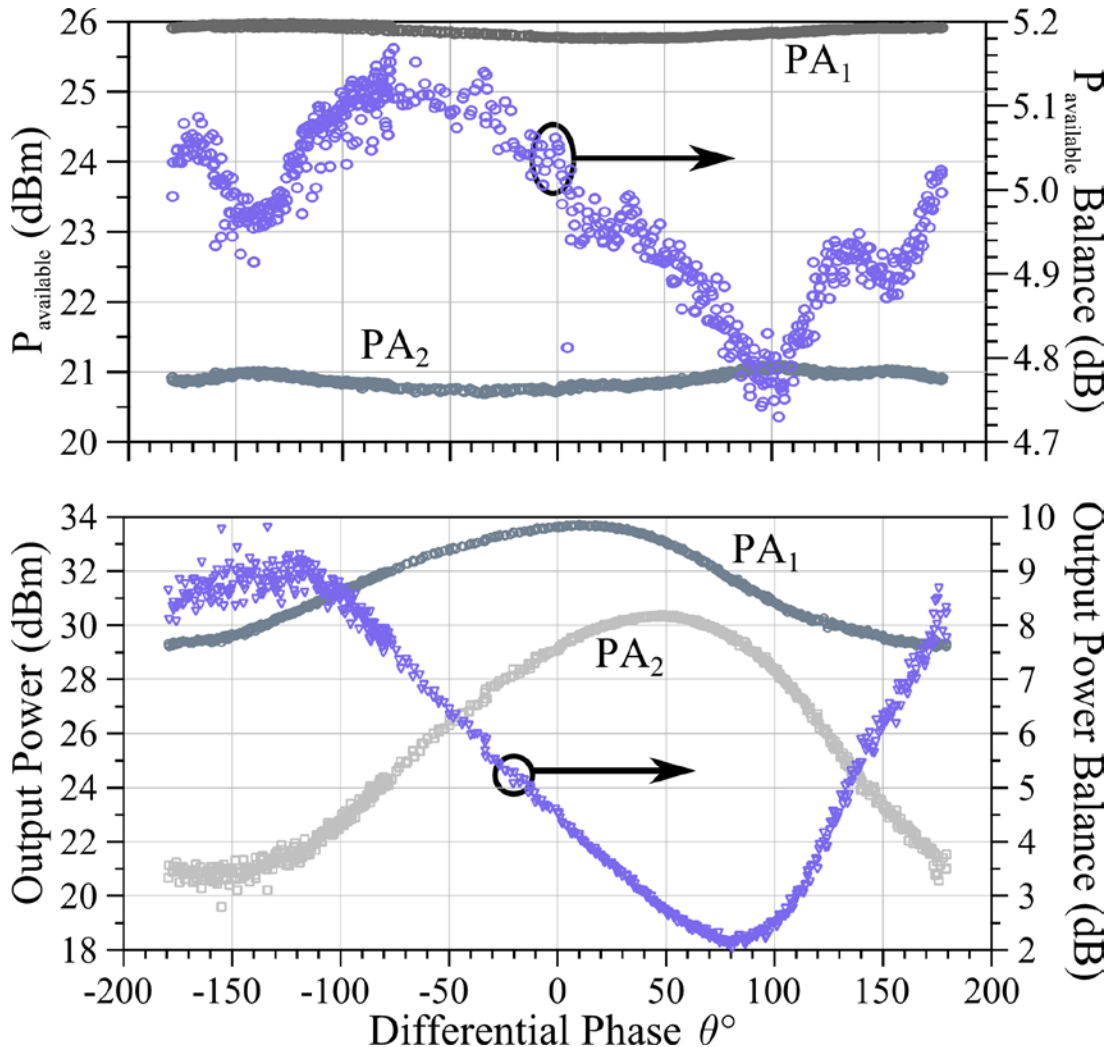

- 5 ± 0.25 dB forced available power imbalance
- 2-9 dB internal PA P_{out} imbalance



Outline



- Overview of approaches for improving efficiency at power back-off
- Supply modulation
 - GaN PA design (10GHz carrier)
 - Supply modulator (100MHz switching)
 - Integration and modeling
- Outphasing
 - Quasi-MMIC isolated and non-isolated
 - Measurements of load modulation internal to the PA
 - Outphasing with supply modulation
- **Discussion and some other challenges**



Doherty

- Simple, not expensive to implement, already accepted
- Broad bandwidth recently demonstrated
- Requires linearization
- Once designed, hardware cannot be modified to fit different signal statistics

Out-phasing

- Efficiency drops quickly with power back-off unless SM is used simultaneously
- Broadband signals require fast digital phase control

Supply modulation

- Requires efficient and fast supply modulator, stability compromised, needs linearization
- Can be digitally modified for different signals




The heat advantage: example S-band PA




- Drive modulated conditions
 - Same W-CDMA signal
 - Same PA
 - Constant 32V V_{dd}
 - Achieves similar linearity
- Power consumption
 - **43% less power**
 - **75% longer from battery**
- Power dissipation
 - **61% less heat**
 - RF transistor operates **86% cooler**

| | Drive (A) | Optimized V_{dd} |
|------------------------|---------------|--------------------|
| Peak/Average Power | 40W / 8.5W | 40W / 8.5W |
| RFPA drain eff. | 30% | 76% |
| SM efficiency | N/A | 69% |
| ACP at 5 / 10MHz | -57/-58.3 dBc | -55.7/-57.8dBc |
| Transmitter efficiency | 30% | 52.5% |
| Supply power | 28.3W | 16.4W |

PA Dissipation
19.8W, 100%

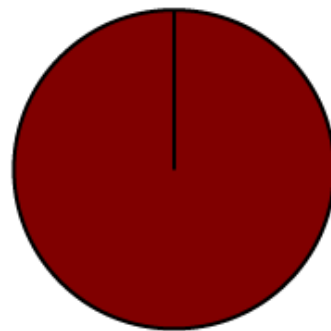

Drive Modulation

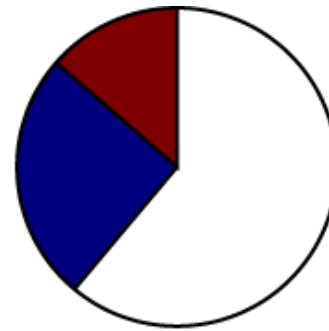




Envelope Tracking

EM Dissipation
5.0W, 25.3%

PA Dissipation
2.7W, 13.6%


Total Dissipation
7.7W, 38.9%

What if the antenna is not matched?

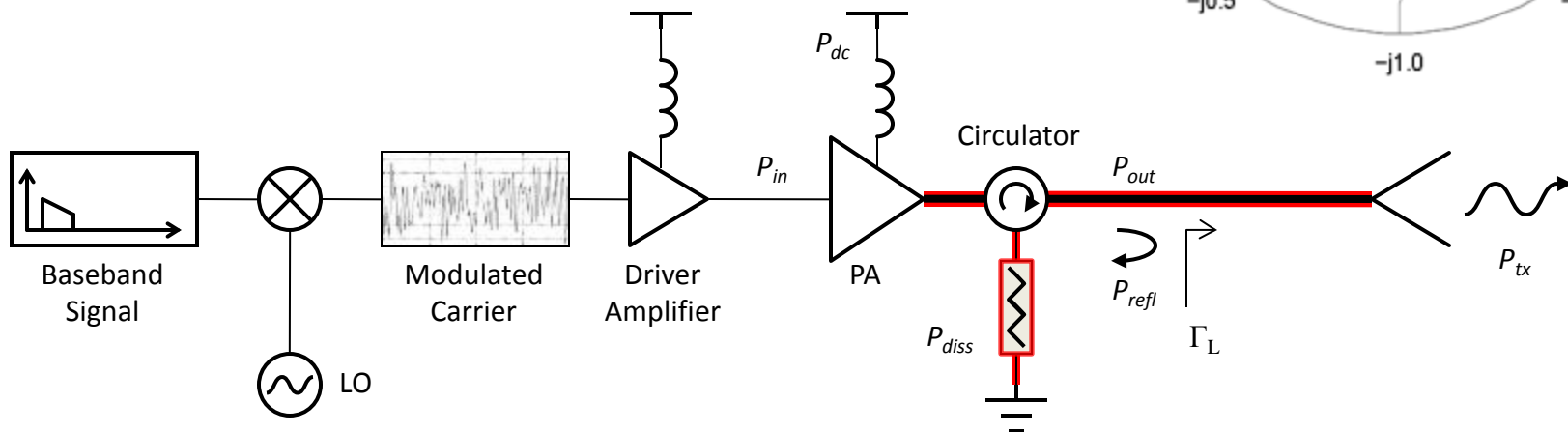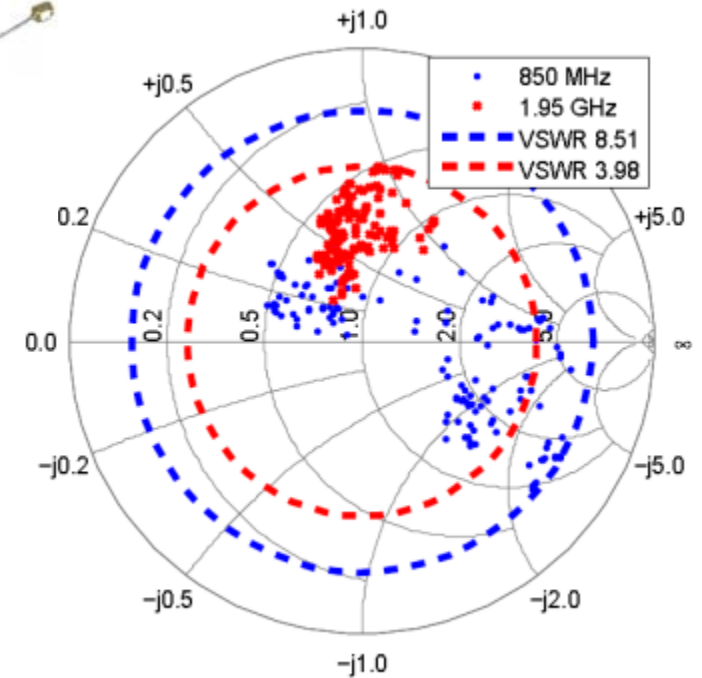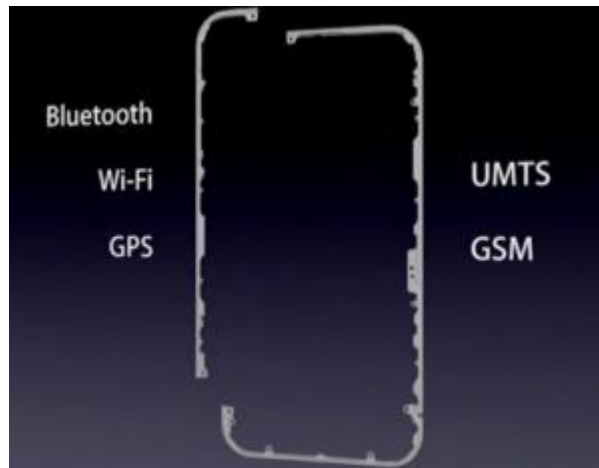



Matching the antenna

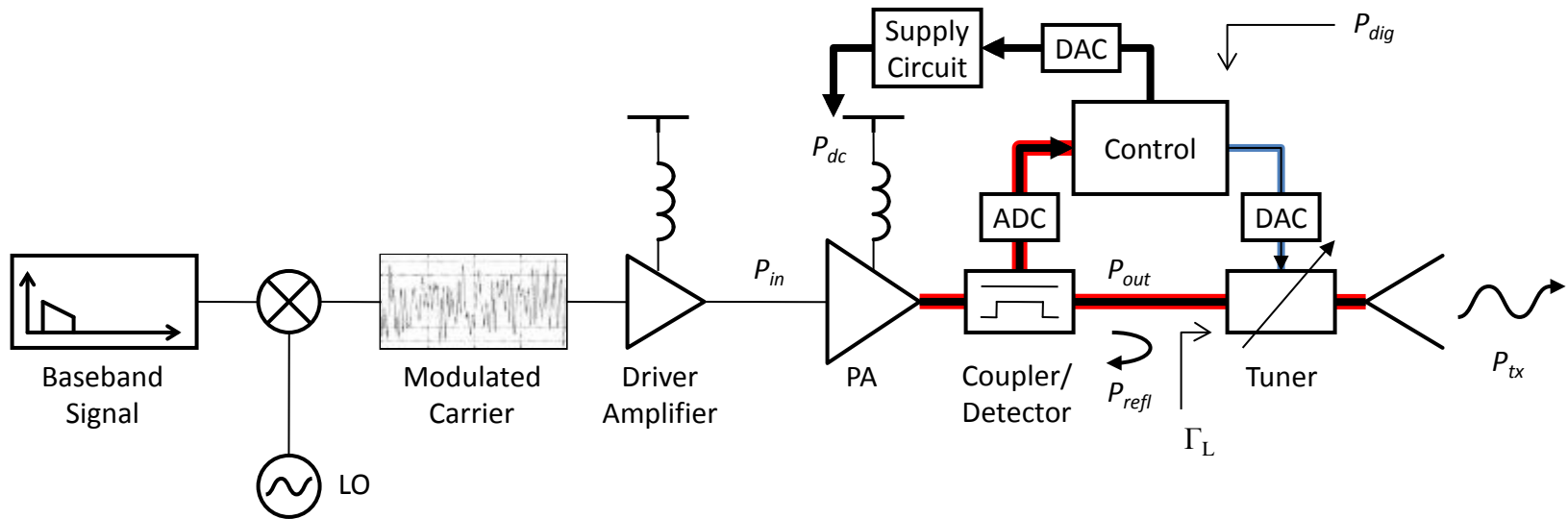

Efficiency improvement

